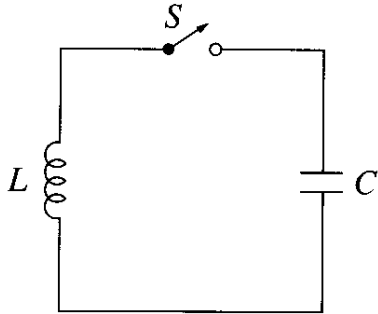


P3323 LC circuit
October 31, 2016

A capacitor C is charged up to a voltage V and connected to an inductor L . At time $t = 0$, the switch S is closed.



1. Find the current in the circuit as a function of time.
2. A resistor R is included in series with C and L . Find the current as a function of time.