
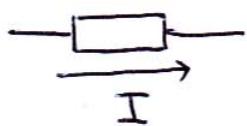


Lecture 2Power

instantaneous power

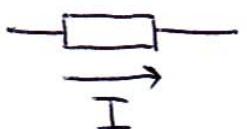


② Voltage Source

or

or

ideal voltage source holds
const voltage no matter what

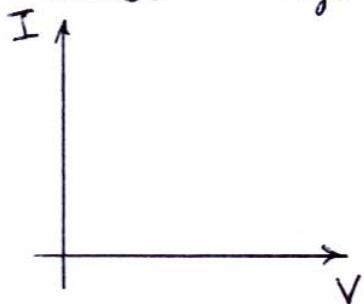Practical volt. source

voltage may not be const


(2)

③ Current source

or

or


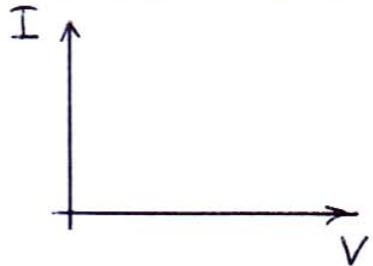
Ideal current source supplies const current no matter what





Practical current source

Circuit analysis

Kirchhoff's voltage law (KVL)

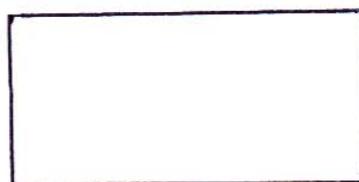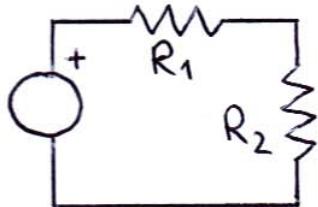


Kirchhoff's current law (KCL)

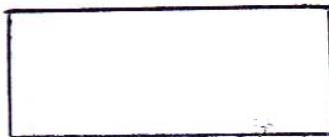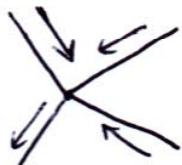


KVL & KCL are completely general

Voltage divider

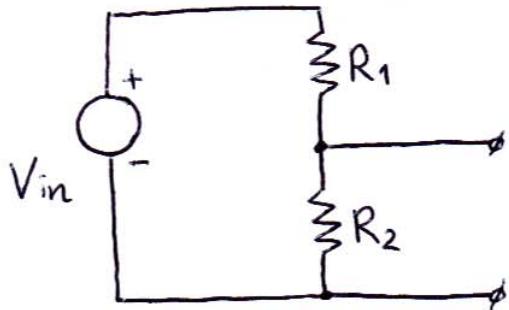

A word on notations

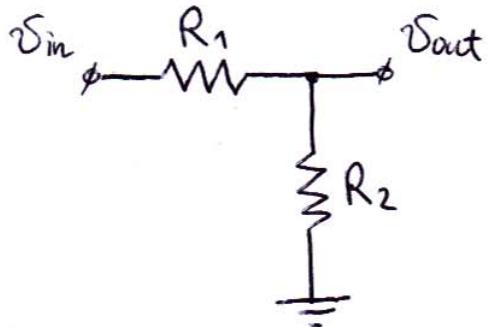

Circuit simplifying techniques

Superposition


Given a _____ circuit containing several i_s , v_s , the total i, v at a given point is algebraic sum from _____ source.

step 1.

step 2.

step 3.



Ex.

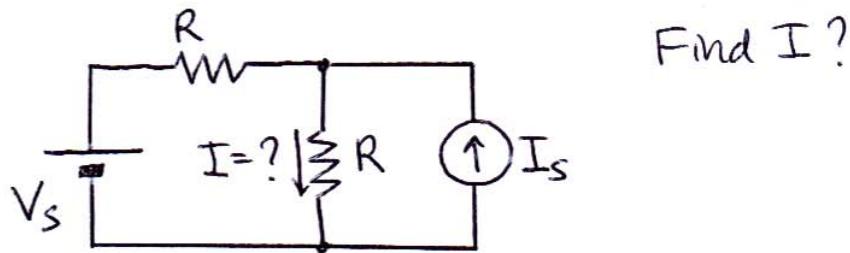

Find I?

① open I_s ② short V_s

③ sum

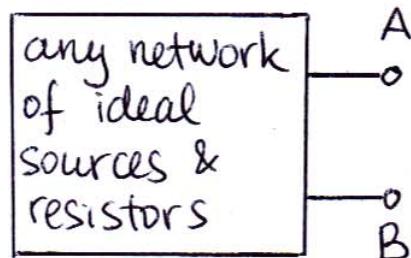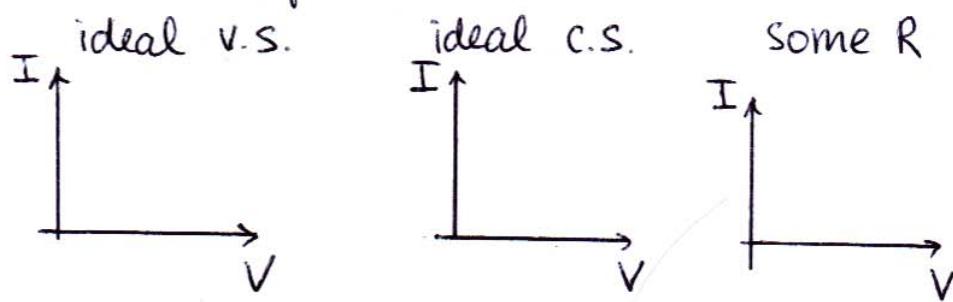Thevenin equivalent

any combination of _____ circuit elements
 with two output terminals may be replaced with
 _____ and _____

$$V_{TH} =$$

$$R_{TH} =$$