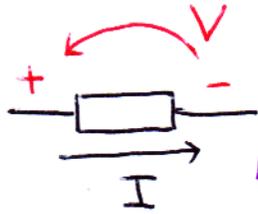


Lecture 2

Power




instantaneous power

$P = IV$

dissipative $P > 0$


resistors are always dissipative

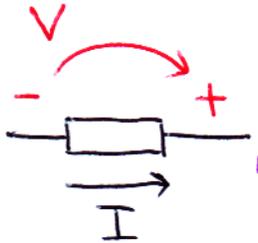


supplies energy $P < 0$

Need elements that supply energy!


② Voltage source

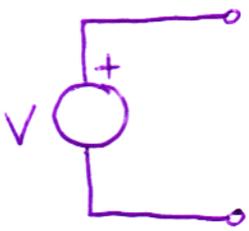

or

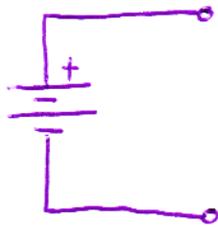


or

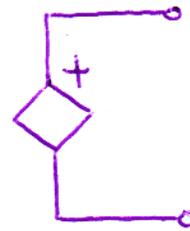

controlled voltage source

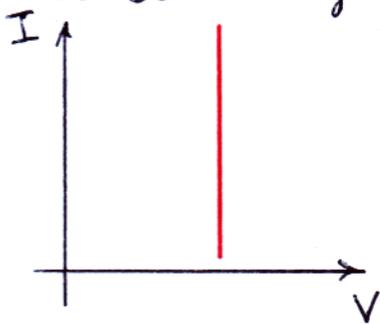
ideal voltage source holds const voltage no matter what



slope = $\infty = \frac{1}{R} \Rightarrow$ slope resistance of ideal volt. source is 0


Practical volt. source

voltage may not be const

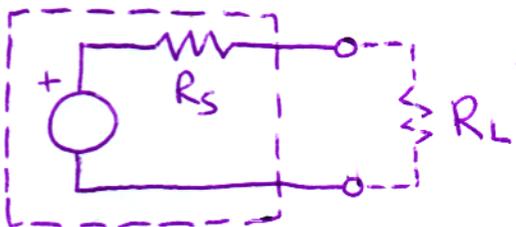


if $R_s \ll R_L \Rightarrow$ close to ideal volt source


3 Current source

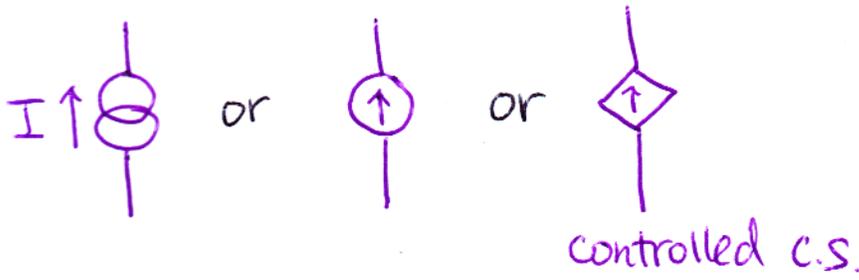

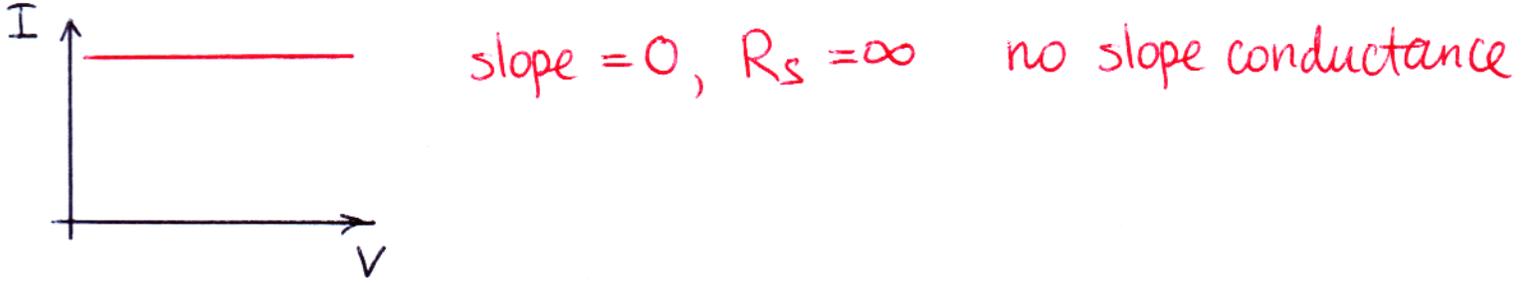Ideal current source supplies const current no matter what




Practical current source

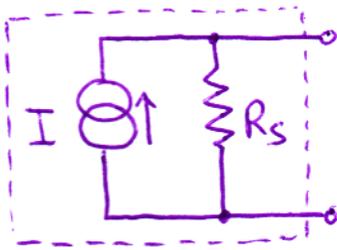

if $R_s \gg R_L \Rightarrow$ close to an ideal current source

Circuit analysis

Kirchhoff's voltage law (KVL)

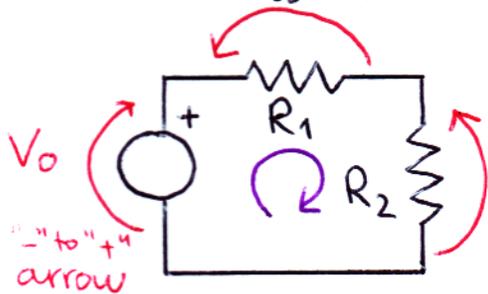

$$\sum V_k = 0$$

around any loop

otherwise ∞ accel.

Kirchhoff's current law (KCL)




$$\sum I_k = 0$$

for any node

conservation of charge

KVL & KCL are completely general (linear & nonlinear dc & ac, etc.) ③


Voltage divider

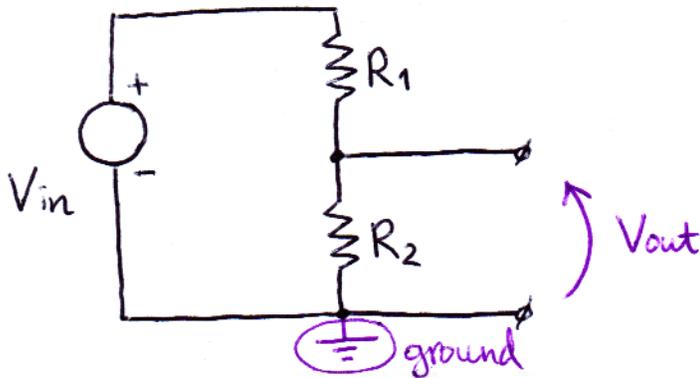

$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2} \quad (\text{memorize})$$

$$V_{out} < V_{in}$$

A word on notations

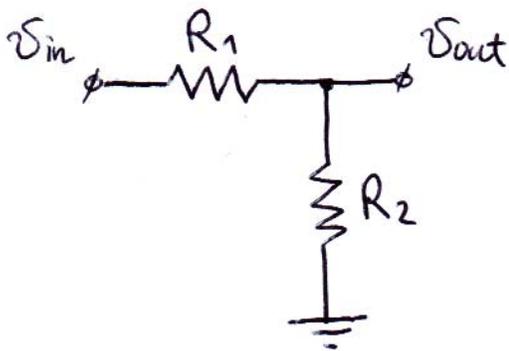

we understand

- ideal volt. source connected between V_{in} & ground
- open circuit ($R_L \rightarrow \infty$) between V_{out} & ground

Circuit simplifying techniques

Superposition

Given a linear circuit containing several i_s , v_s , the total i , v at a given point is algebraic sum from each individual source.


step 1. For each $(i_s)_k$ or $(v_s)_k$: replace all other v_s with shorts and i_s with open circuit

step 2. compute i_k and v_k


step 3. sum $v = \sum_k v_k$ and $i = \sum_k i_k$

Ex.

Find I?

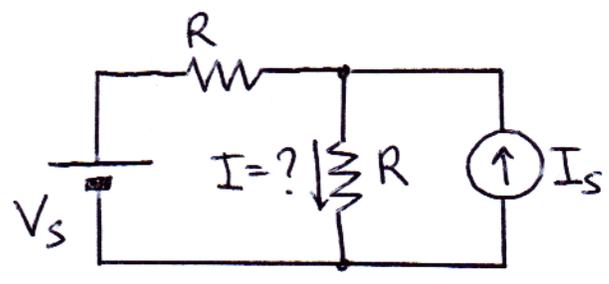


① open I_s

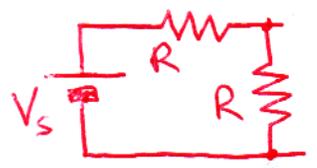

$$I_1 = \frac{V_s}{2R}$$







② short V_s

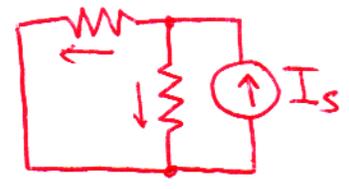

$$I_2 = \frac{I_s}{2}$$

③ sum $I = \frac{V_s}{2R} + \frac{I_s}{2}$

Thevenin equivalent

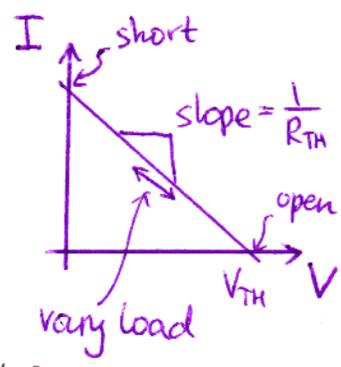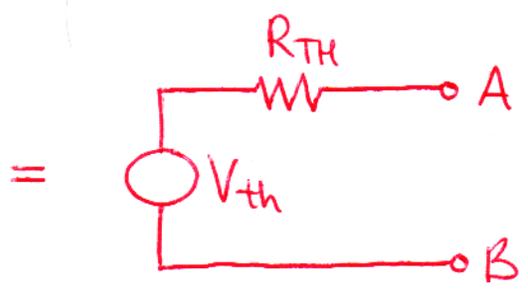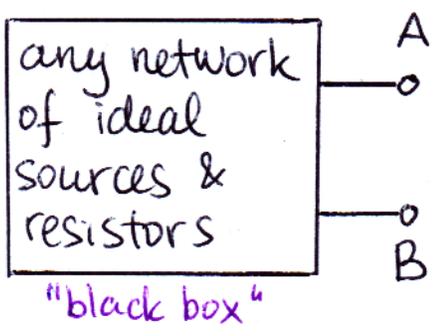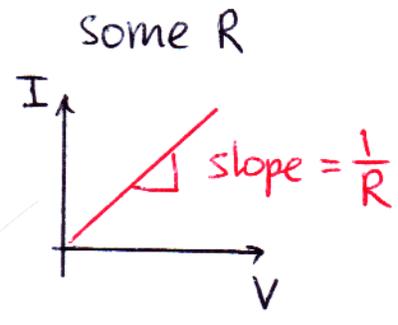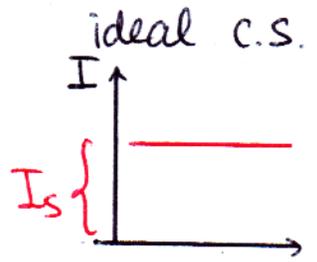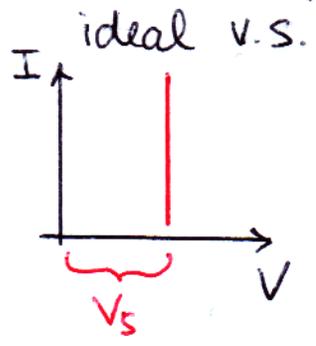

any combination of linear circuit elements with two output terminals may be replaced with ideal volt. source and series resistance

$$V_{TH} = V_{o.c.}$$

$$R_{TH} = \frac{V_{o.c.}}{I_{s.c.}}$$