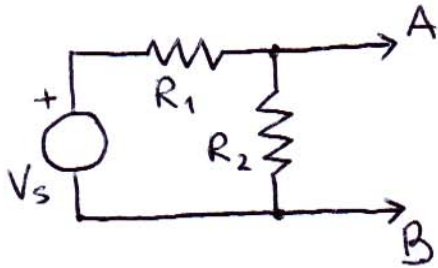


Lecture 3

Thevenin th. - example



Useful trick: to find R_{Th} , short _____ and open _____. R_{Th} is resistance by looking inside the two terminals.

Norton equivalent

same as Thevenin but \Rightarrow

$$I_N = \quad , R_N =$$

Linear time-dep. elements

(2)

Linear if KVL & KCL contain terms \propto
but never

(4) Capacitor




2 parallel plates
separated by
insulator

$$Q =$$


$$[C] = \text{farads}$$

$$C_{\text{Total}} =$$
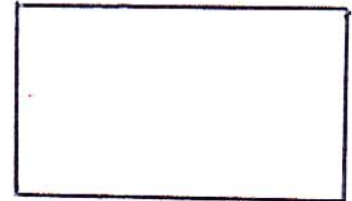
$$V = \frac{Q}{C}, \Rightarrow \frac{dV}{dt} =$$



(5) Inductors


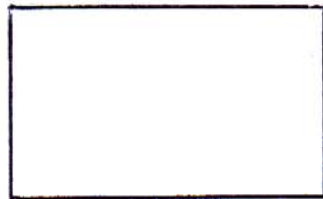


$$[L] = \frac{V \cdot s}{A} = \text{henries}$$

$$L_{TOTAL} =$$

Bulky \approx MHz, not routinely used

Low - Pass filter

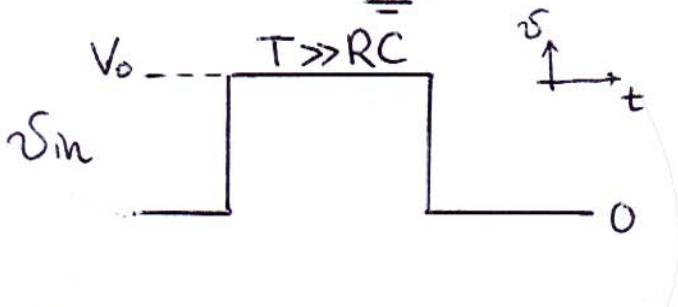
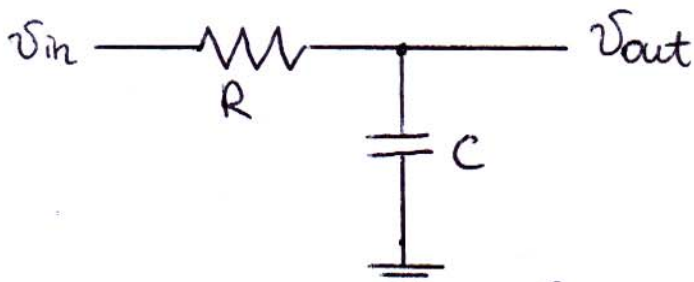


v_out


v_R

Piece of trivia:
v_c vs t after
step in voltage

High-pass filter

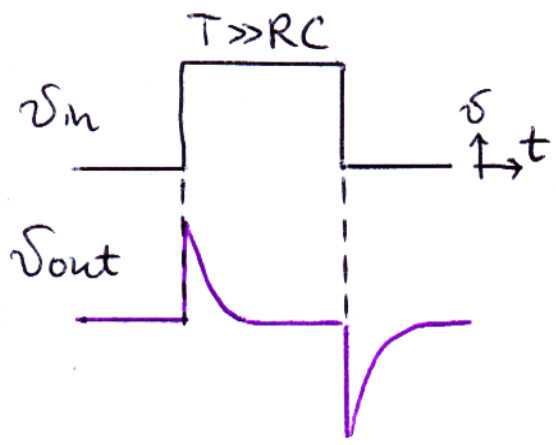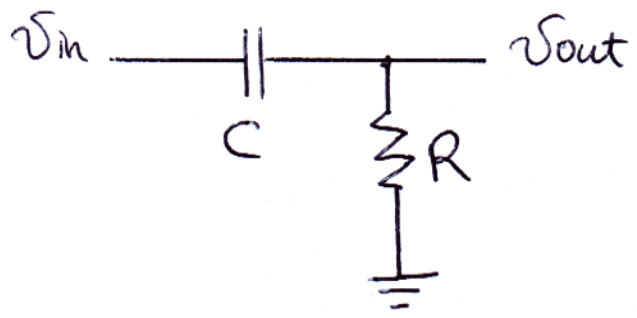

Exp I-10

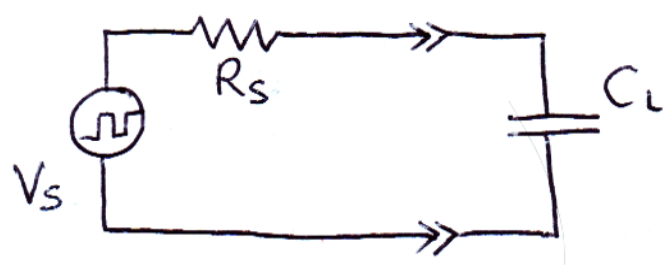

Function generator produces \square , \wedge , \sim
drives capacitive load C_L

input \square

\Rightarrow output

'Fake' large R_i by adding large R to f -generator.

Need to transmit shape. How?

Soln.