

Lecture 4

Amplifiers

-

-

- many applications

-

-

Symbol

Characteristics


① Gain

decibels

Q: why dB?


$G = v_{out} / v_{in}$	$G_{dB}$
1	0 dB
$\sqrt{2}$	+3 dB
2	+6 dB
10	+20 dB
$\frac{1}{10}$	-20 dB

② Input resistance

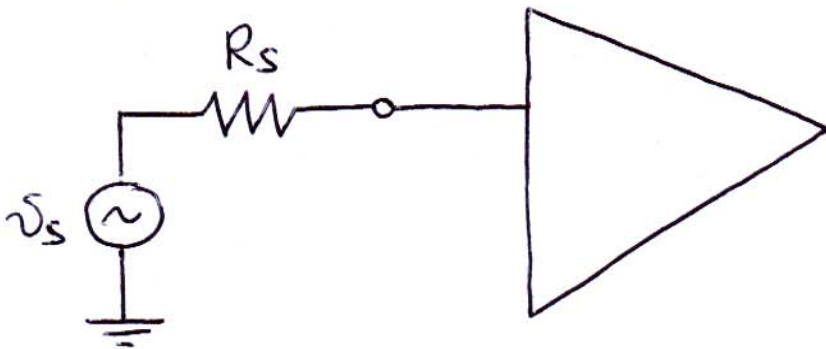


Q: what input impedance is ideal?

③ Output impedance

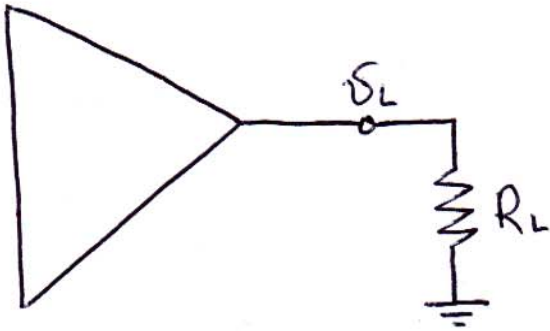


Input types

a) single input

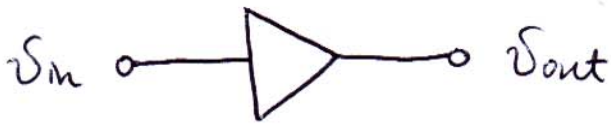



b) differential

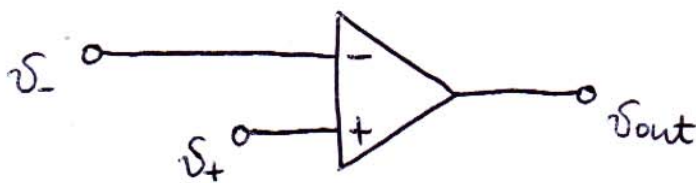

# Operational amplifier

④

-  
-

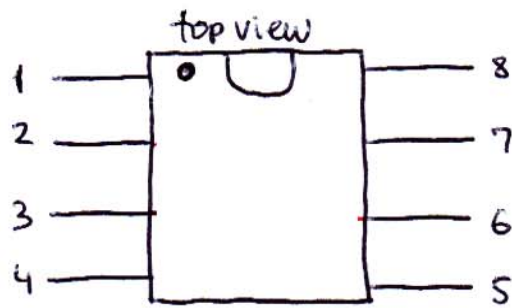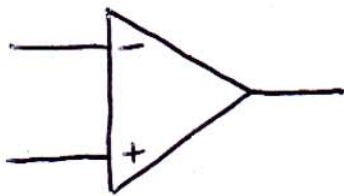


741 and 3140 op-amps used in the lab

## Manufacturer spec sheets

- everything you need to know about an IC
- see PDF's on the course web-site / books in the lab

## Powering op-amp


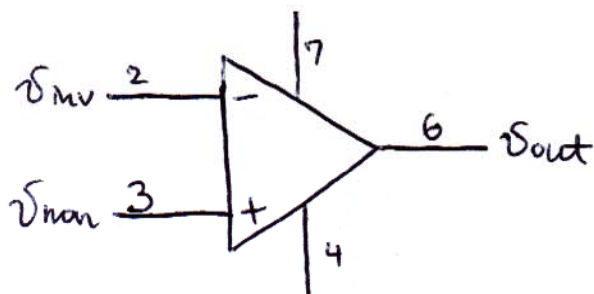


-  
-  
-  
-

Lecture 5

Op-amp characteristics

Gain

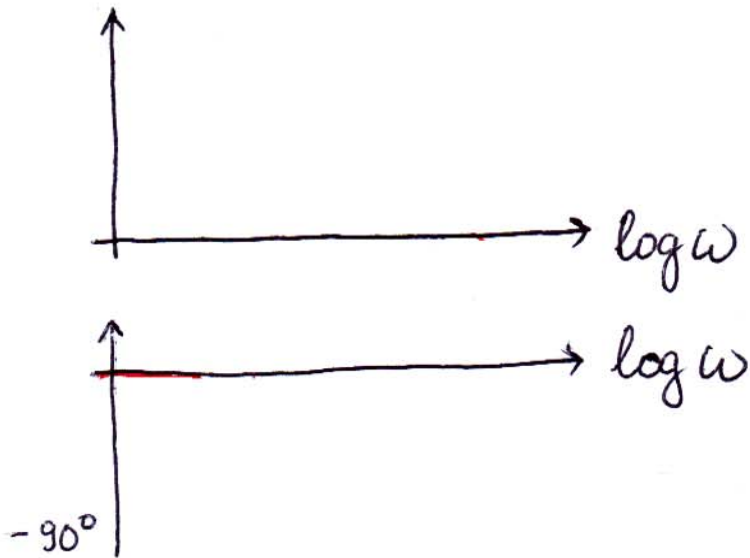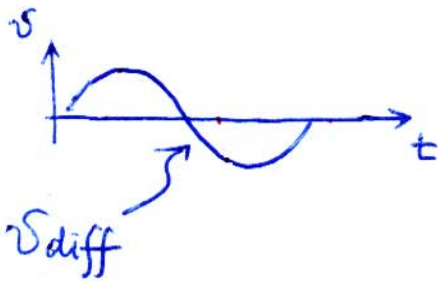



Typically

$$G =$$

Unity gain bandwidth



# Transfer characteristic

(2)

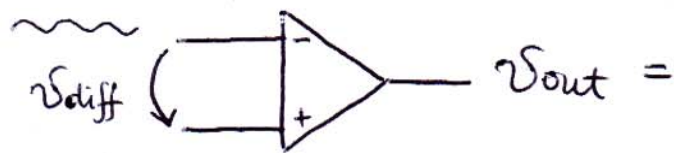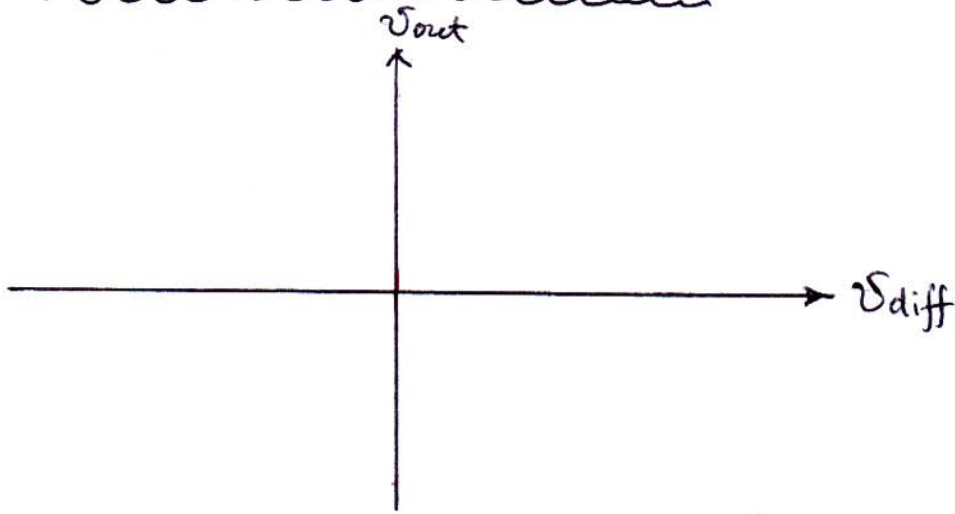


- bare op-amp is a \_\_\_\_\_ amplifier

# Input offset voltage

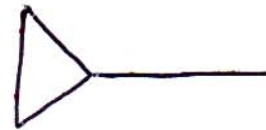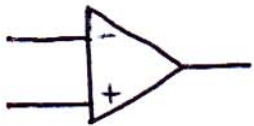

# Stew rate & propagation delay

3

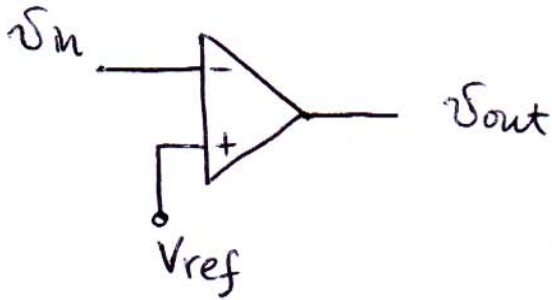

## Ideal op-amp



- 1) input draw \_\_\_\_\_
- 2) output resistance
- 3)  $V_{sat+} =$   
 $V_{sat-} =$
- 4)  $G \sim \infty$
- 5)  $V_{os} \rightarrow 0$ ,  $S.R. \rightarrow \infty$ ,  $T_{p.d.} \rightarrow 0$

- always start with \_\_\_\_\_, then apply non-ideal properties \_\_\_\_\_.

# Op-amp circuits

(4)

## Comparator

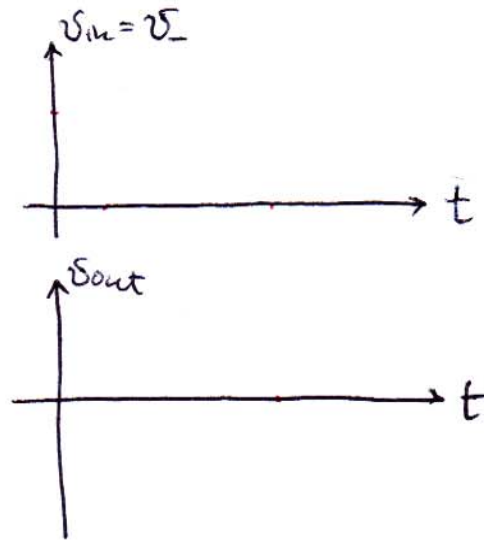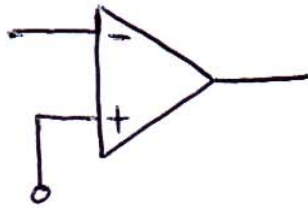

analog signal in

---

- comparator =



problems with comparator

soln.:



Lecture 6

Schmitt trigger

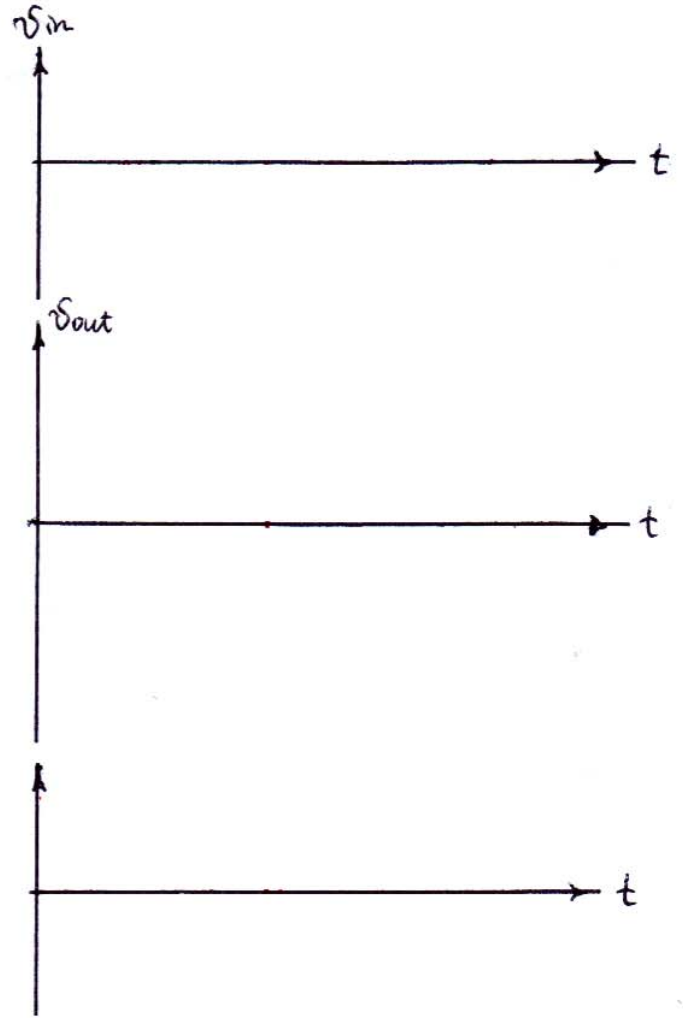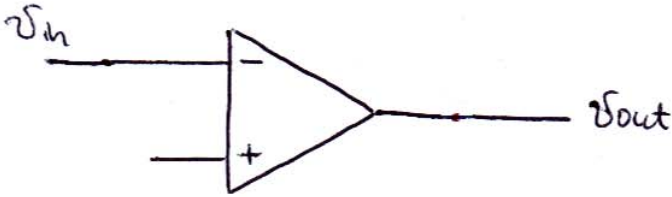


- this is an example of \_\_\_\_\_

- positive feedback \_\_\_\_\_ the current trend through whisking the threshold

# Transfer characteristic


②

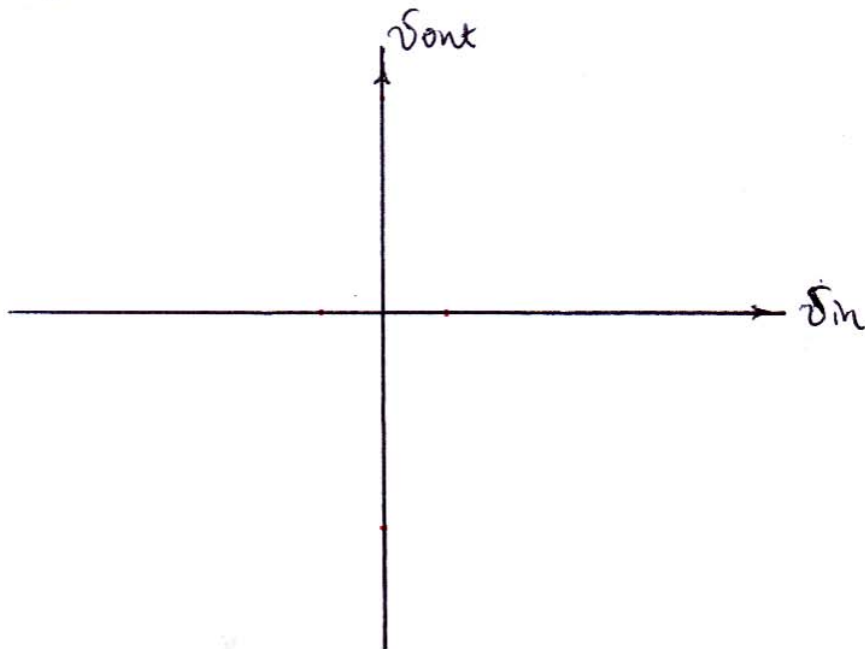

- threshold now depends \_\_\_\_\_

# Astable multivibrator

③

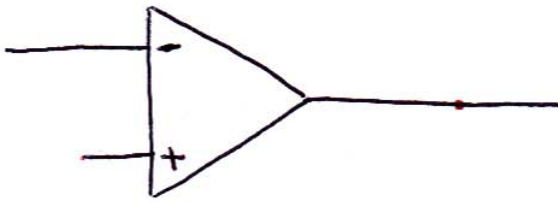


- op-amp supplies




Strategy for solving unknown circuits :

Starting oscillations :

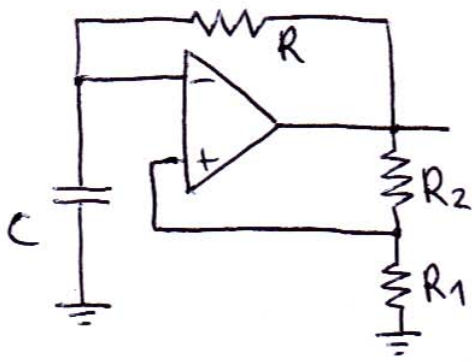- assume ideal op-amp
- there is always noise, so  $v_+ = v_-$  is never true for long



Analyze oscillator  
voltage vs time

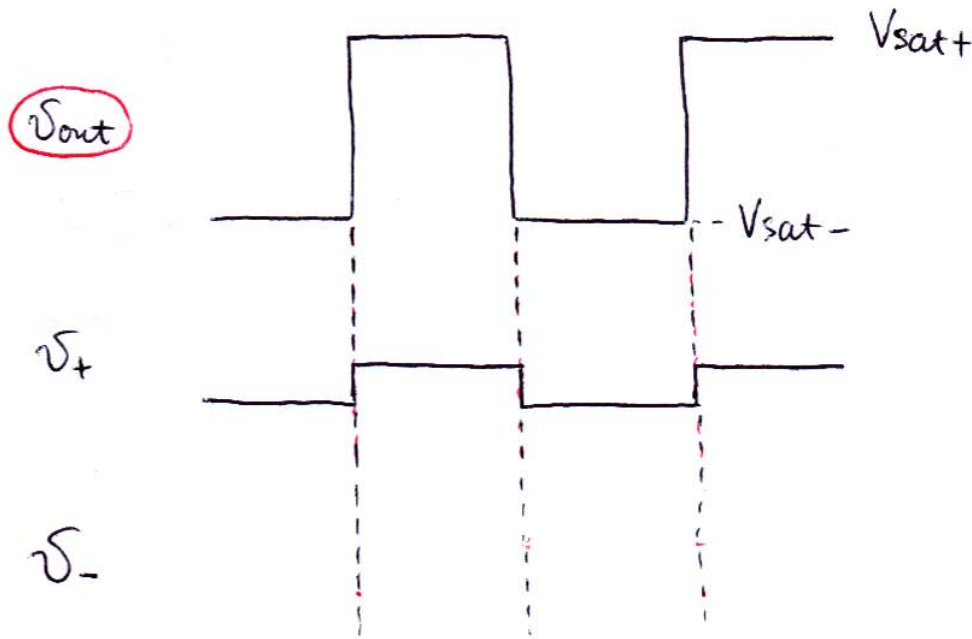

For simplicity  $V_{sat+} = |V_{sat-}| = V_{sat}$

$$v_c(\Delta t) = V_F + (V_I - V_F) e^{-\frac{\Delta t}{RC}} \quad (*)$$

$$V_I = \quad , \quad V_F =$$

$$v_c(\Delta t) =$$