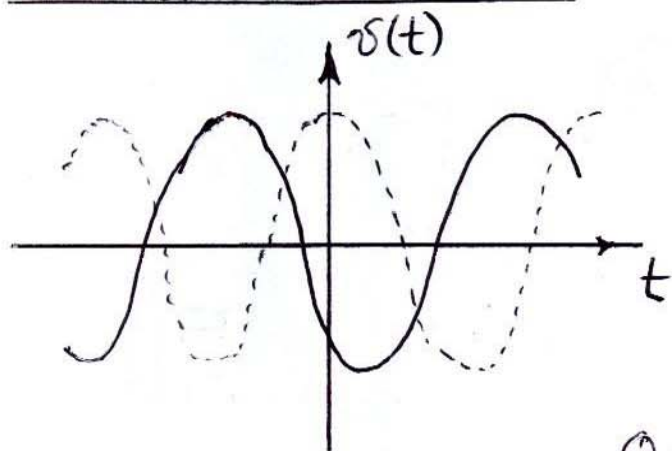


Lecture 7Linear AC circuits

$$v(t) = V_0 \cos(\omega t + \phi)$$

Q: why study AC (sine) response?


1)

Q: if you have _____ network, what shape on input remains the same on the output?

2)

3) superposition:

Complex notation

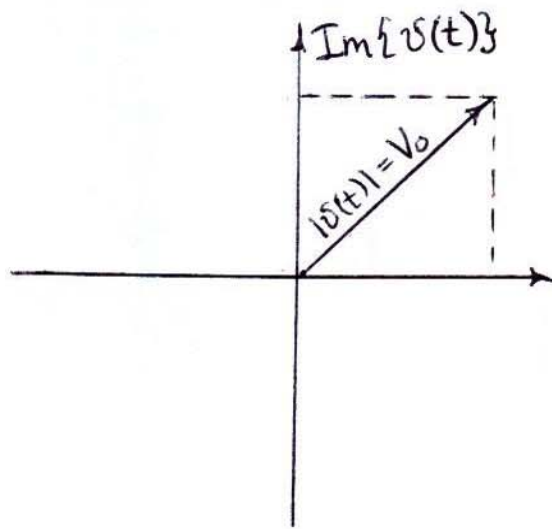

Euler formula

$$e^{j\alpha} = \cos\alpha + j\sin\alpha$$

$$j^2 = -1$$

$$v(t) =$$

Usually simply write $v(t) =$

Time vs. freq. domain analysis

Time domain: $v(t), i(t)$

KVL & KCL $\Rightarrow$

—

—

Freq. domain: $V(\omega), I(\omega)$

$$\frac{d}{dt}(e^{j\omega t}) \rightarrow$$

$$\int e^{j\omega t} dt \rightarrow$$


KVC & KCL $\Rightarrow$

③



- two ways to look
- Fourier analysis :

Complex impedance

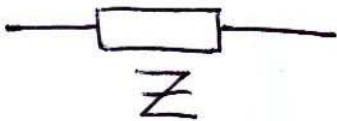

$$V(\omega) =$$

admittance = generalized conductance

$$\text{Let } i(t) = I_0 e^{j\omega t}, \quad v(t) = V_0 e^{j(\omega t + \phi)}$$

$$Z(\omega) =$$

Impedance can change both _____ ④

$$Z = R + jX = Z_0 e^{j\varphi}, \Rightarrow$$

Capacitance

$$\frac{d\psi}{dt} = \frac{i}{C}$$

$$Z_C = \frac{\psi(t)}{i(t)} =$$

voltage _____ current by 90°

Inductance

$$\psi = L \frac{di}{dt}$$

$$Z_L = \frac{\psi(t)}{i(t)} =$$

voltage _____ current by 90°

→ i

	$\omega \rightarrow 0$	$\omega \rightarrow \infty$
Z_R		
Z_L		
Z_C		