

Lecture 8Combining R, L, C

series: $Z_T = Z_1 + Z_2 + \dots$ (add impedances)

parallel: $Y_T = Y_1 + Y_2 + \dots$ (add admittances)

Similar to combining R's, but now add & manipulate complex numbers

E.g.





Q: is current through R, L, C different?

A: no, it is the same (KCL)

$$Z_{AB} = R + \frac{1}{j\omega C} + j\omega L \quad (\text{E complex})$$

$$V_{AB}(\omega) = Z_{AB} \cdot I_{AB}(\omega)$$

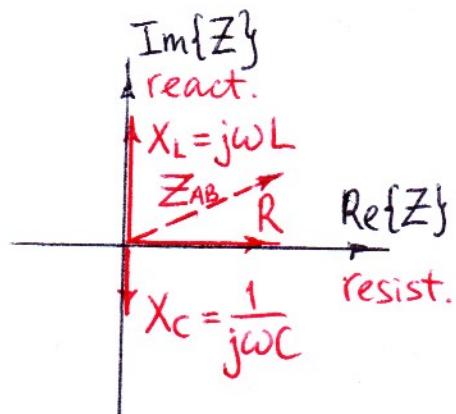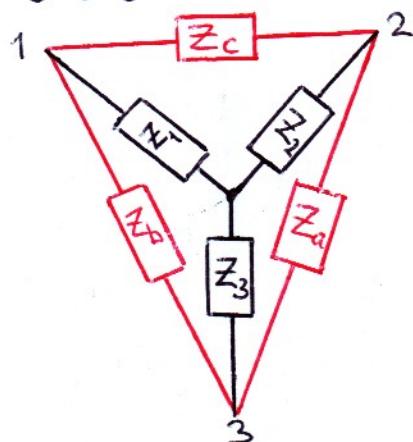 Δ -Y transformation

same as before, but now complex

$$\Delta \rightarrow Y: Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}, \dots$$

$$Y \rightarrow \Delta: Y_a = \frac{Y_2 Y_3}{Y_1 + Y_2 + Y_3}, \dots$$

AC circuit analysis




②

* superposition YES (if linear)

Q: which apply?
* Thevenin & Norton YES (if one freq.)

* KCL & KVL YES
(always)

Lo-pass filter (revisited)

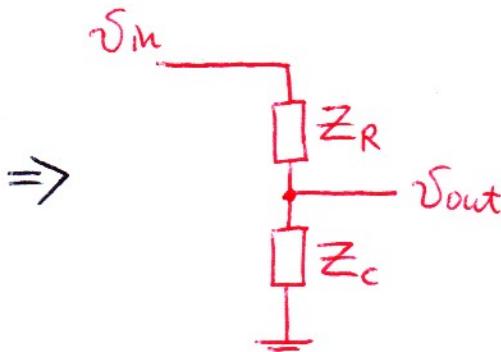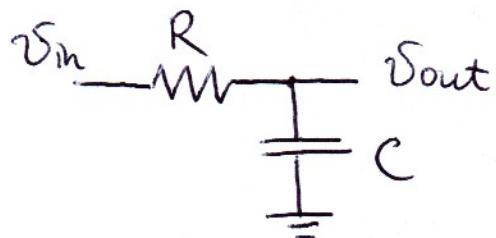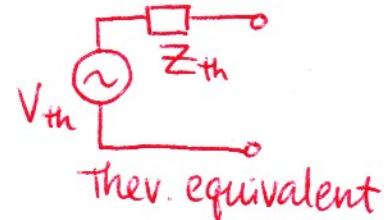

Q: looks familiar?
A: Yes, volt. divider!

Transfer fcn (a.k.a. complex gain)

$$G(\omega) \equiv \frac{V_{out}(\omega)}{V_{in}(\omega)}$$

$$\text{L.P. : } G(\omega) = \frac{V_{in} \cdot Z_c}{Z_c + Z_R} \frac{1}{V_{in}} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC}$$

Q: $C = \frac{A}{B}$, magn & phase?

$$|C| = \frac{|A|}{|B|}, \Phi[C] = \Phi[A] - \Phi[B]$$

$$\text{magn. } |G(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\begin{aligned} \text{phase } \Phi[G] &= \Phi[1] - \Phi[1 + j\omega RC] \\ &= -\tan^{-1}(\omega RC) \end{aligned}$$


- | can be measured
- | by network analyzer
- | VNA - vector NA
both magn & ph
- | SNA - scalar NA
only magn.

(3)

Bode plots

$$G(\omega) = |G(\omega)| e^{j\varphi[G(\omega)]}$$

Bode plots = plot $|G|$ and φ versus ω
 (log-log) (semi-log)

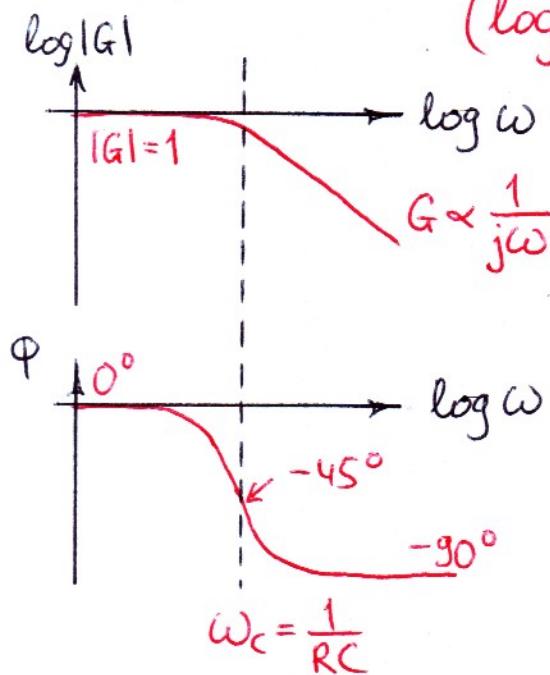


$$\omega_c = \frac{1}{RC} \quad \begin{cases} \omega \ll \omega_c, G \approx 1 \\ \omega \gg \omega_c, G \approx \frac{\omega_c}{j\omega} \end{cases}$$

"corner freq"

$$Q: \text{phase?} \quad \begin{cases} \omega \ll \omega_c & 0^\circ \\ \omega \gg \omega_c & -90^\circ \end{cases}$$

Usually draw uncorrected Bode plots.

use dB for $|G|$ and deg. for φ

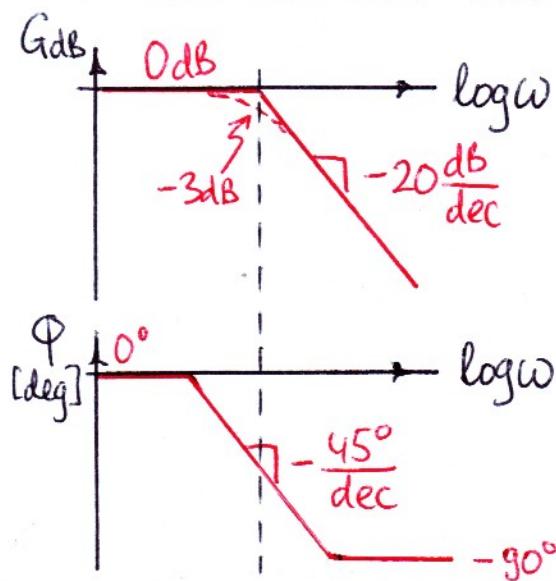

To make Bode plots:
 mentally sweep through all freq.

$$G(\omega_c) = \frac{1}{1+j}, \Rightarrow$$


$$|G(\omega_c)| = \frac{1}{\sqrt{2}} \text{ or } -3\text{dB}$$

$$\varphi[G(\omega_c)] = -45^\circ$$



$$\text{decade: } \frac{\omega_2}{\omega_1} = 10 \quad \text{octave: } \frac{\omega_2}{\omega_1} = 2$$

$$20 \text{ dB/dec} = 6 \text{ dB/oct}$$

Hi-pass filter

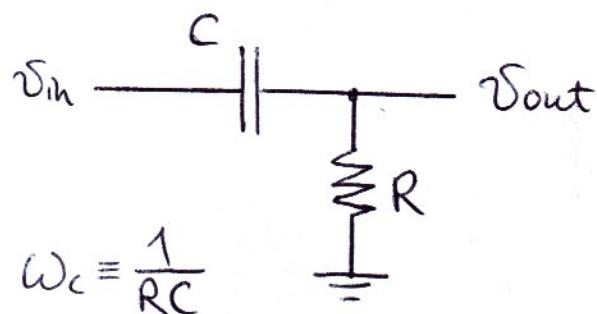
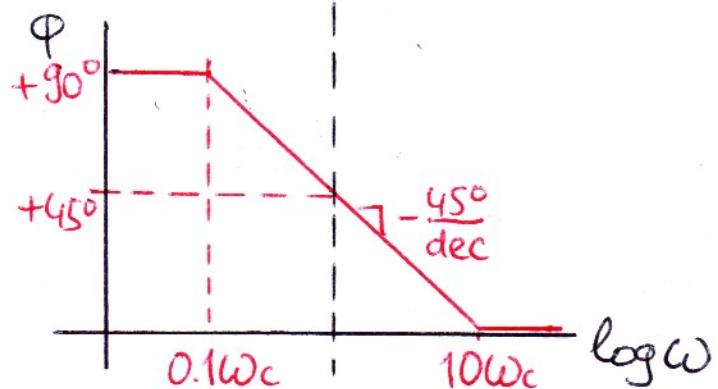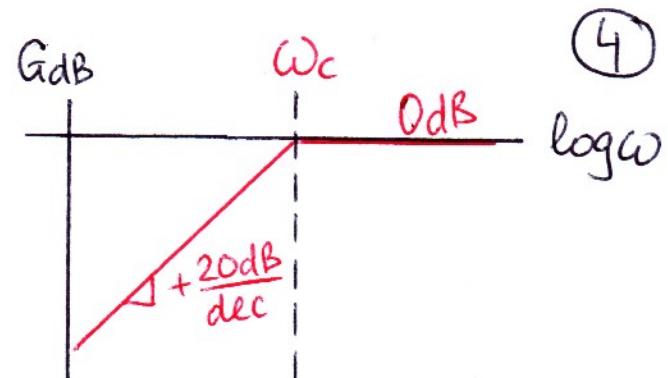
$$G(\omega) = \frac{Z_R}{Z_R + Z_C} = \frac{j\omega/\omega_c}{1 + j\omega/\omega_c}$$



Note: Bode plots \Rightarrow always two

$$G(\omega) = |G(\omega)| e^{j\Phi[G(\omega)]}$$

$$\ln G(\omega) = \ln |G(\omega)| + j\Phi[G(\omega)]$$

real imag

- magnitude & phase are not independent
- e.g. change in magn. requires change in phase
(a.k.a. Kramers-Kronig relation)

Standard (zero-pole) form of G

$$G(\omega) = \frac{N(\omega)}{D(\omega)} = K(j\omega)^n \frac{(1+j\omega/\omega_{z_1})(1+j\omega/\omega_{z_2})\dots}{(1+j\omega/\omega_{p_1})(1+j\omega/\omega_{p_2})\dots}$$

$N(\omega \rightarrow j\omega_z) \rightarrow 0, |G| \rightarrow 0$ called zero

$D(\omega \rightarrow j\omega_p) \rightarrow 0, |G| \rightarrow \infty$ called pole