

Lecture 10

Negative FeedbackGood amp :


- $R_{in} \gg R_s$
- $R_{out} \ll R_L$
- $G(\omega) = \text{const}$

"Bare" op-amp problems :

- small active range
- large G variations
- $G \propto \frac{1}{\omega}$ for $\omega_c \gg 10\text{Hz}$
- R_{out} is fairly large

$$v_{out} =$$

②

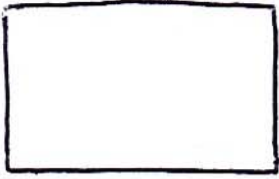

- throw away _____ to make
a stable circuit, indep. of _____

Advantages of negative F.B.



①

②



$$(v_m)_{active} =$$

3

3

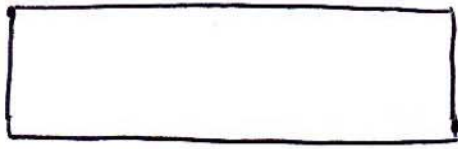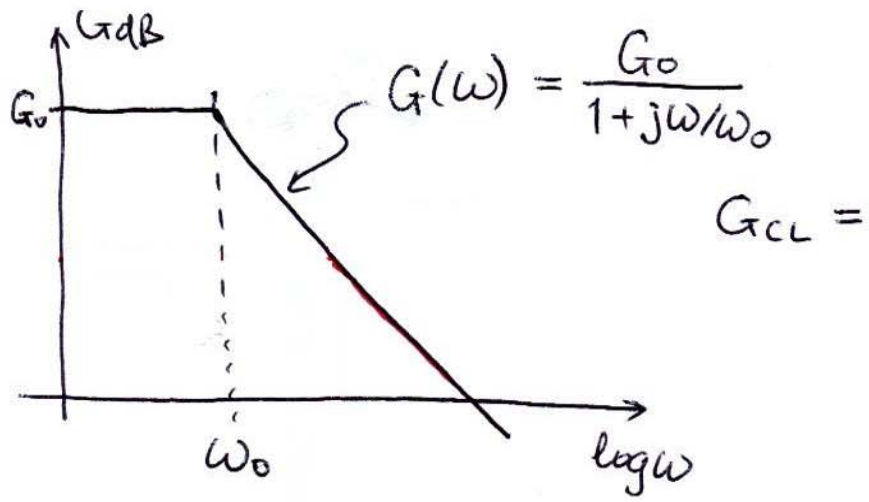

4

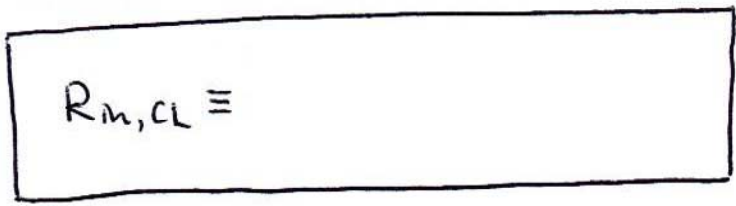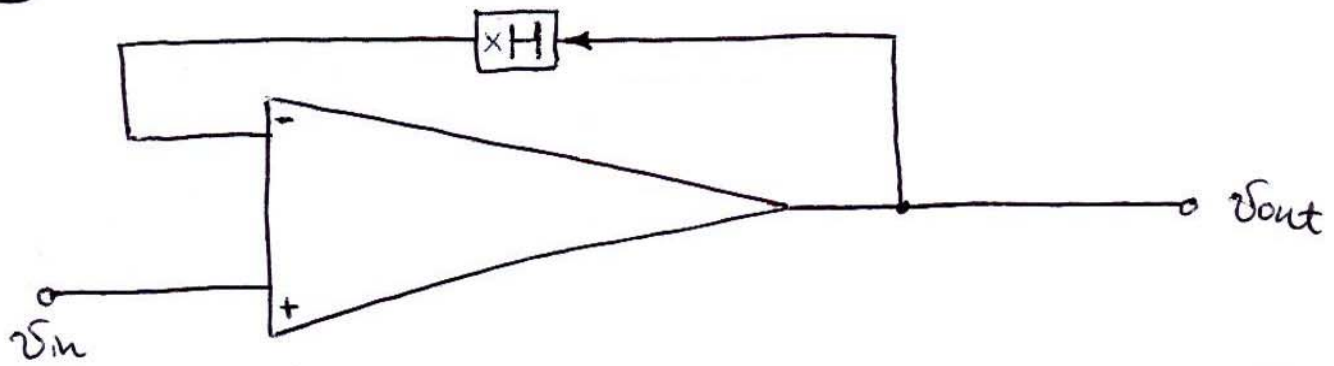

⑤

$$V_{out} =$$

$$V_{out} =$$

$$R_{out, CL} =$$

④

Rules for analyzing negative F.B. circuits

- 1) current rule:
- 2) voltage rule: