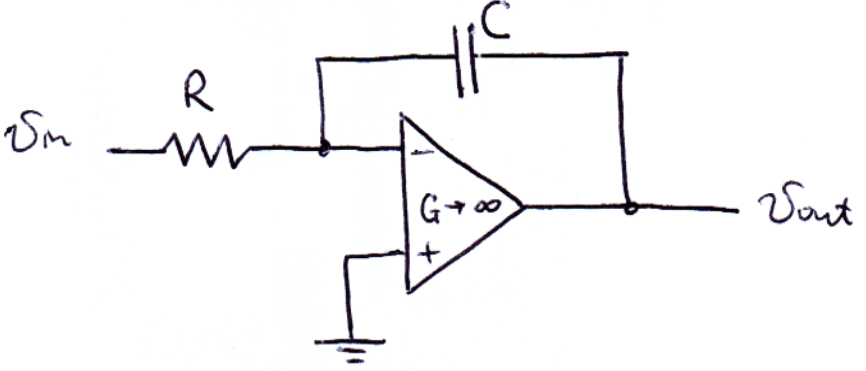


P3360/AEP3630

Lecture 12

Integrator

$$v_{out} \propto \int v_{in} dt \Rightarrow G_{cl}(s) \propto$$





AC response :


$$G_{cl}(\omega) =$$

Problem 1 :

Problem 2 :

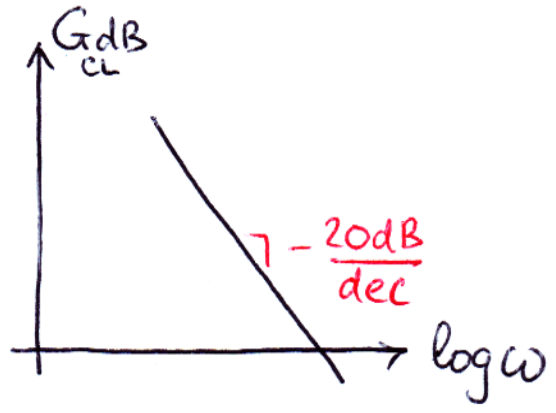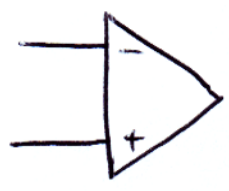


Leaky integrator

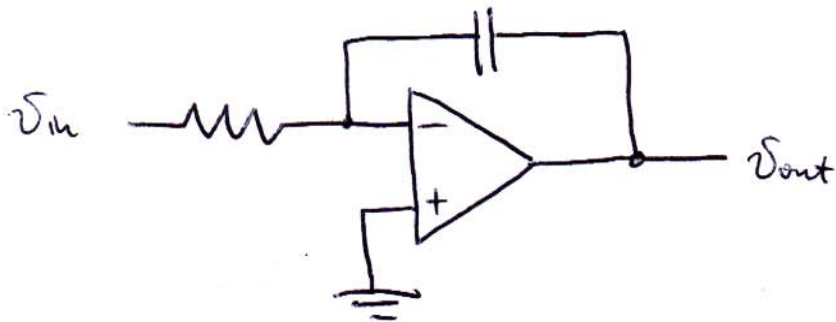

$$G_{CL}(\omega) \approx$$

$$G_{CL}(\omega) =$$

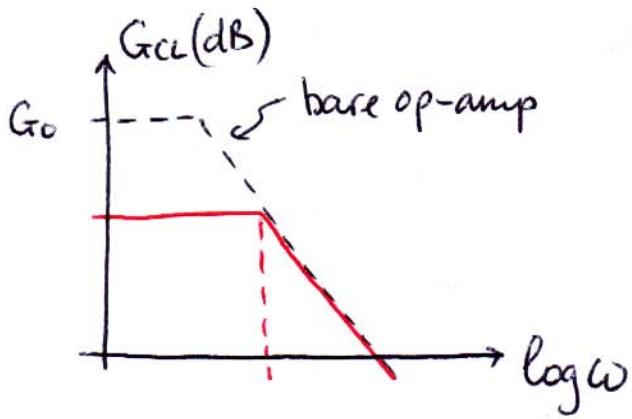


Pros:

Cons:

Differentiator

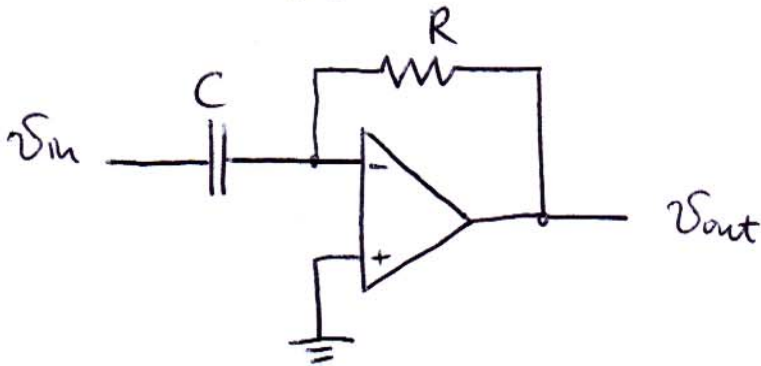
$$v_{out} \propto \frac{d}{dt} v_{in} \quad , \Rightarrow \quad G_{CL}(s) \propto$$





AC response:

$$G_{CL}(\omega) =$$

Problem :

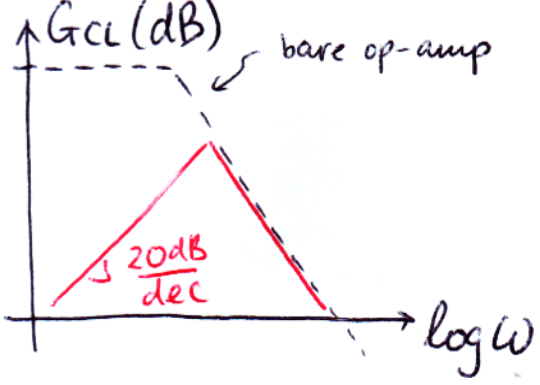



Soln :

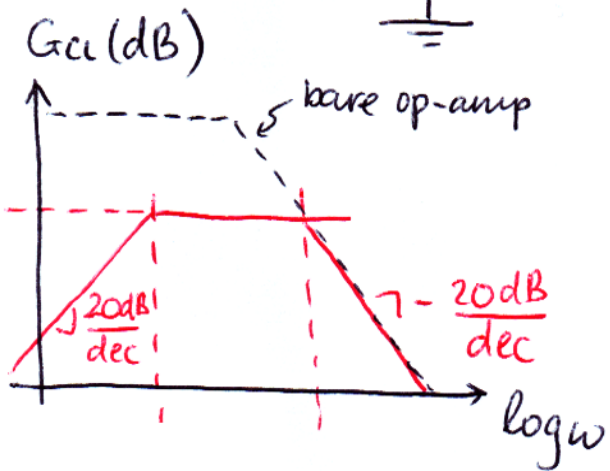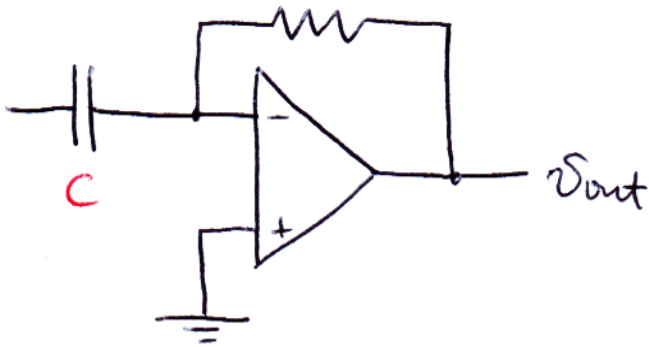

Pros:

Cons:


Stability

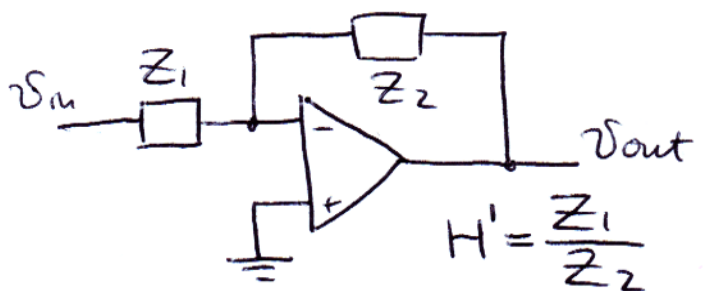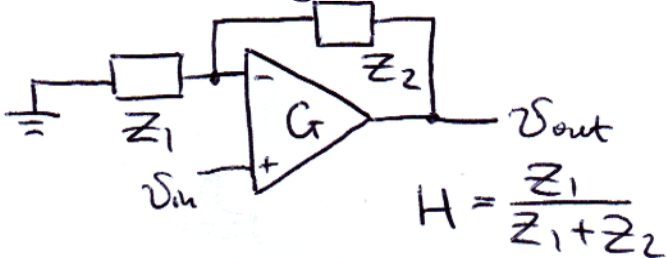


$$G_{CL} = \frac{1}{H} \frac{1}{1 + \frac{1}{GH}}$$

$$G_{CL} = -\frac{1}{H'} \frac{1}{\left(1 + \frac{1}{G}\right) + \frac{1}{GH'}} \quad (4)$$

Phase & gain margins

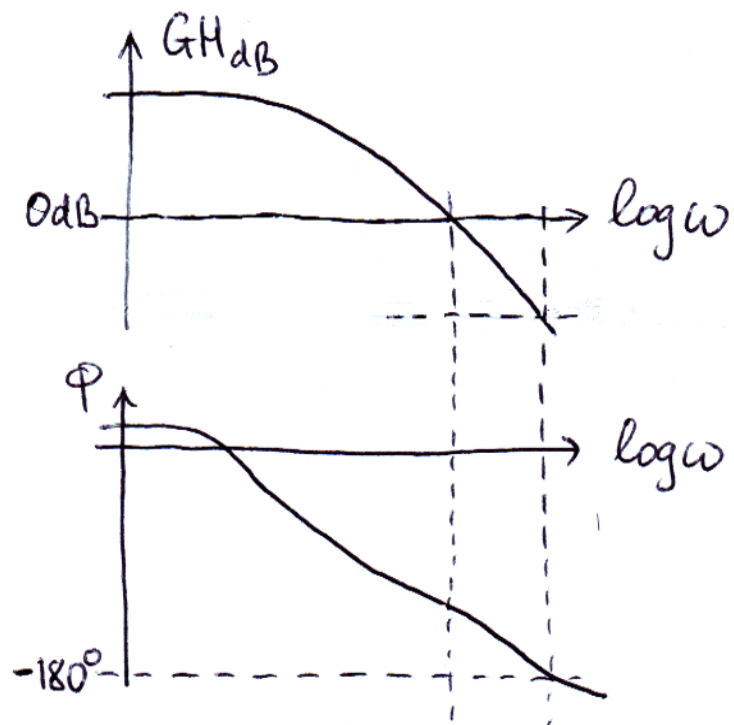

Nyquist plots

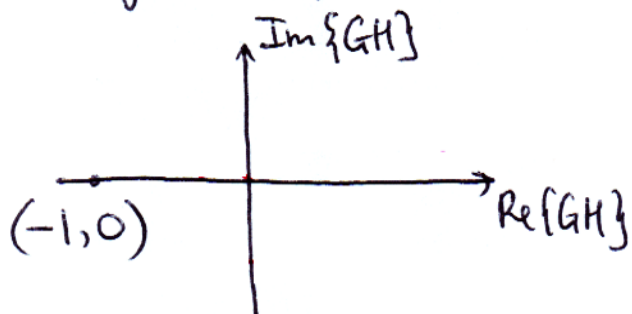

Nyquist criterion of stability: