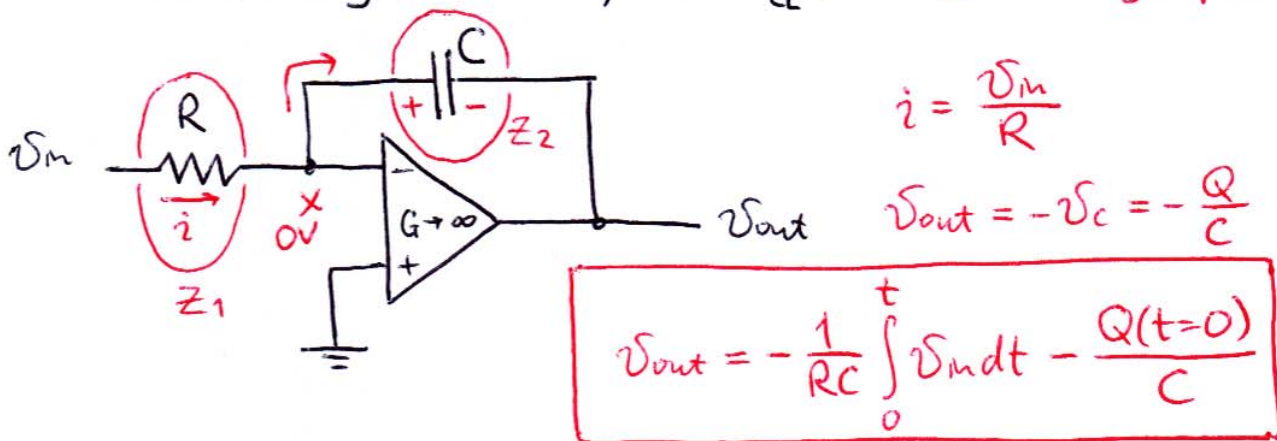


P3360/AEP3630

Lecture 12

Integrator

$v_{out} \propto \int v_{in} dt, \Rightarrow G_{cl}(s) \propto \frac{1}{s}$ single pole @ origin




AC response :

$G_{cl}(\omega) = \frac{v_{out}}{v_{in}} = -\frac{Z_2}{Z_1} = -\frac{1}{j\omega RC}$, or $G_{cl}(s) = -\frac{1}{sRC}$


Problem 1: $G_{cl}(\omega \rightarrow 0) \rightarrow \infty$?

ω_{cl} depends on G_0

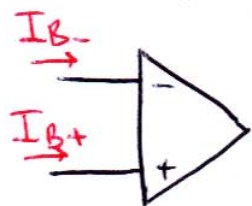Problem 2: I_B needed to bias transistors inside op-amp.



e.g. 741 $|I_B| \sim 20nA$
314D $|I_B| \sim 10pA$

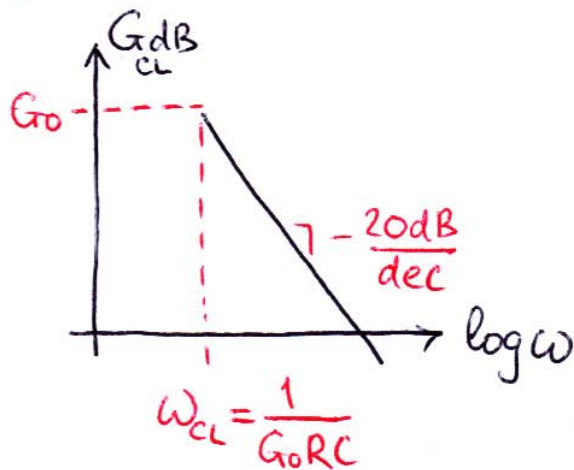


\Rightarrow will charge the cap / offset DC

Solution


(2)

Leaky integrator

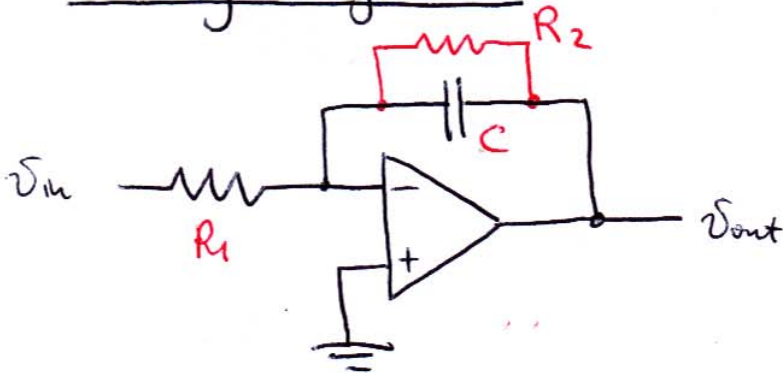

$$G_{CL}(\omega) \approx -\frac{R_2 \parallel Z_C}{R_1}$$
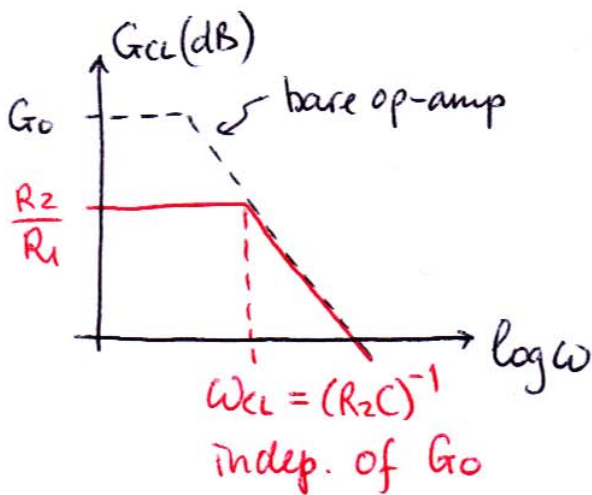
$$G_{CL}(\omega) = -\frac{R_2}{R_1} \frac{1}{1+j\omega R_2 C}$$




Pros: fixed Probs 1 & 2

Cons: integrates only $\omega \gg \omega_{CL} = (R_2 C)^{-1}$

Differentiator

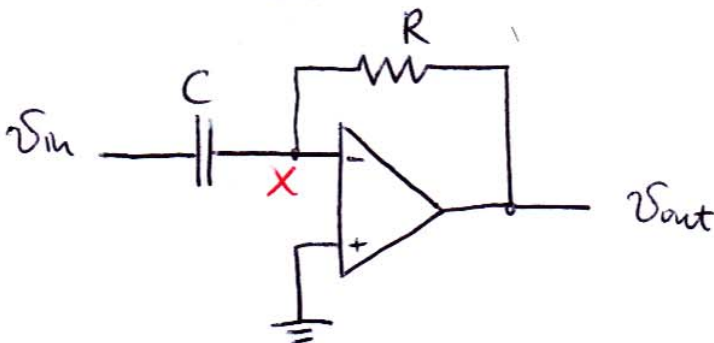$v_{out} \propto \frac{d}{dt} v_{in}$, $\Rightarrow G_{CL}(s) \propto s$ single zero @ origin




$$v_{in} = v_C = \frac{Q}{C}$$

$$i = \frac{dQ}{dt} = C \frac{dv_{in}}{dt}$$

$$v_{out} = -iR = -RC \frac{dv_{in}}{dt}$$

AC response:
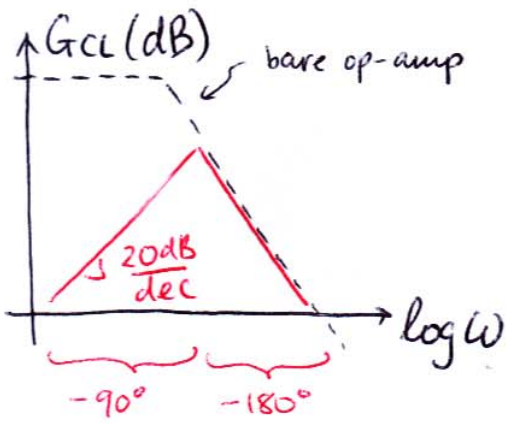
$$G_{CL}(\omega) = -\frac{R}{1/j\omega C} = -j\omega RC, \text{ or } G_{CL}(s) = -sRC$$



Problem: output may "ring" (3)

Q: why?


F.B.: -90° phase lag

op.-amp: -90° phase lag (comp.)

$\Rightarrow -180^\circ$ total phase lag,


"-" is turned into "+" F.B. (oscillations)

Soln:

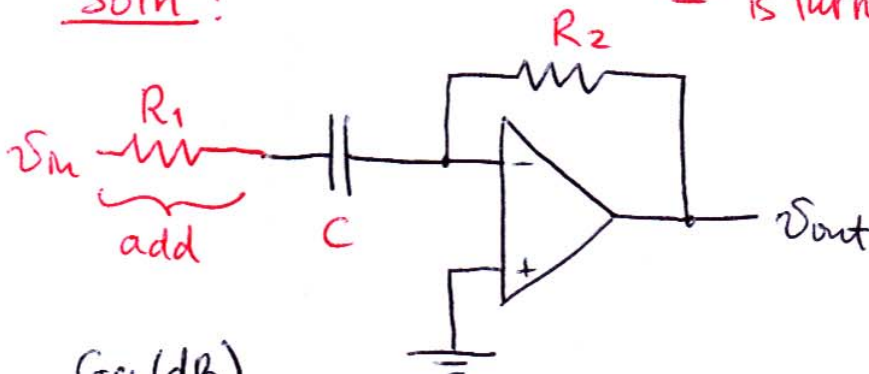

assuming $G_{OL} \rightarrow \infty$
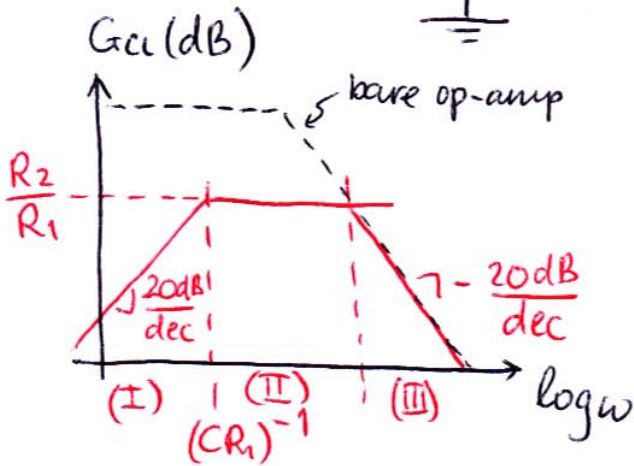
$$G_{cl}(\omega) = -R_2 \frac{j\omega C}{1 + j\omega C R_1}$$



(I) -90° phase lag

(II) bring phase back to 0°

(III) int. comp.: -90° phase lag



Pros: no 180° phase change

\Rightarrow no "+" F.B.

Cons: differentiates only

$$\omega \ll (C R_1)^{-1}$$

Stability

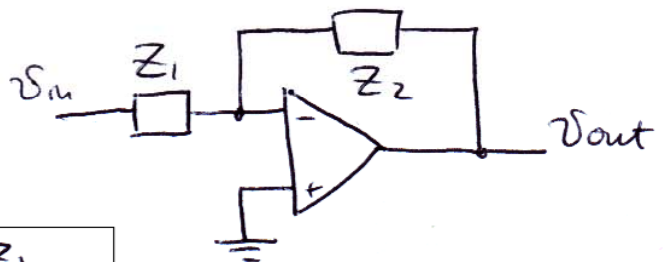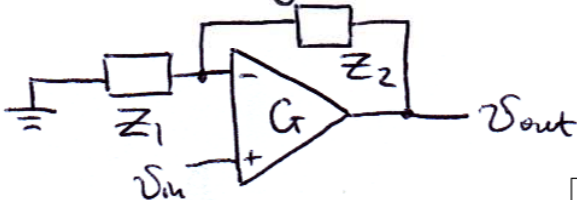

$$H = \frac{Z_1}{Z_1 + Z_2}$$

$$G_{CL} = \frac{1}{H} \frac{GH}{1+GH}$$

$$G_{CL} = -\left(\frac{1}{H} - 1\right) \frac{GH}{1+GH} \quad (4)$$

$GH = \text{loop gain} = |GH|e^{j\phi}$


If @ some freq $\phi = \pm 180^\circ$, $GH = -|GH|$

\Rightarrow turn negative into positive F.B.

if $|GH| < 1$ @ $\phi(\omega) = -180^\circ$, \Rightarrow may ring but will damp

if $|GH| > 1$ @ $\phi(\omega) = -180^\circ$, \Rightarrow self-sustained oscillations

Phase & gain margins

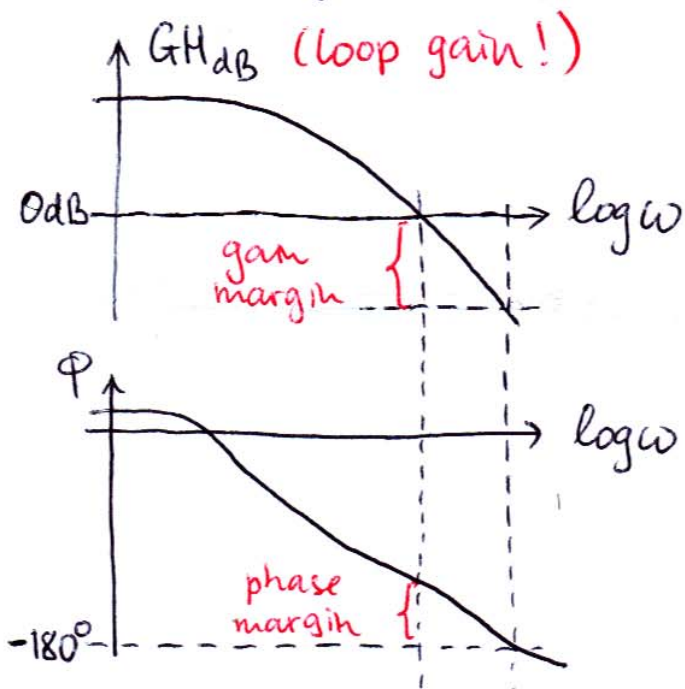

$$G_{CL} = \frac{1}{H} \frac{GH}{1+GH} = 0 \quad (\text{stay away from!})$$

if $GH = -1$


Rule of thumb for loop gain:

phase margin $> 45^\circ$

gain margin $> 10-12dB$

Nyquist plots

plot $GH(\omega)$ on complex plane

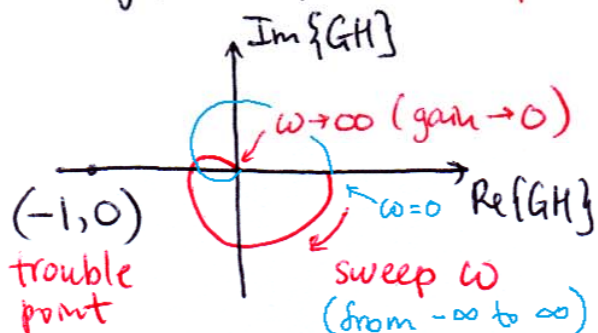

Nyquist criterion of stability:

if Nyquist curve encompasses $(-1, 0)$

\Rightarrow circuit is unstable