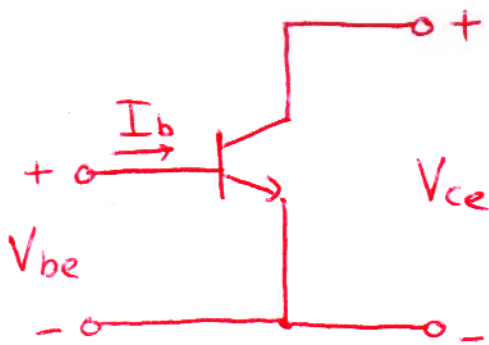


Lecture 16

Transistors (BJT's)

3 terminals \Rightarrow one terminal common to input & output


Common emitter configuration (one of 3 possibilities)



$$V_{be} \equiv V_b - V_e$$

$$V_{ce} \equiv V_c - V_e$$


input characteristics

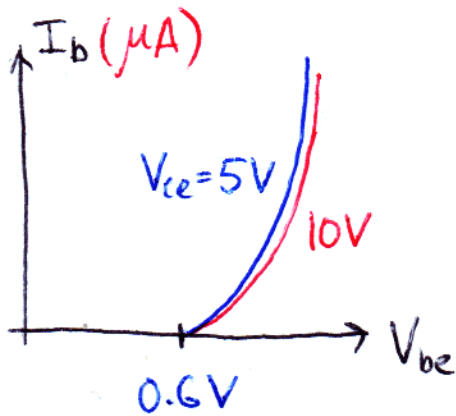

- like forward biased diode
- weak dependence on V_{ce}

output (3 modes)

	be-junct.	bc-junct.
I cutoff	reverse	reverse
II active	forward	reverse
III satur.	forward	forward

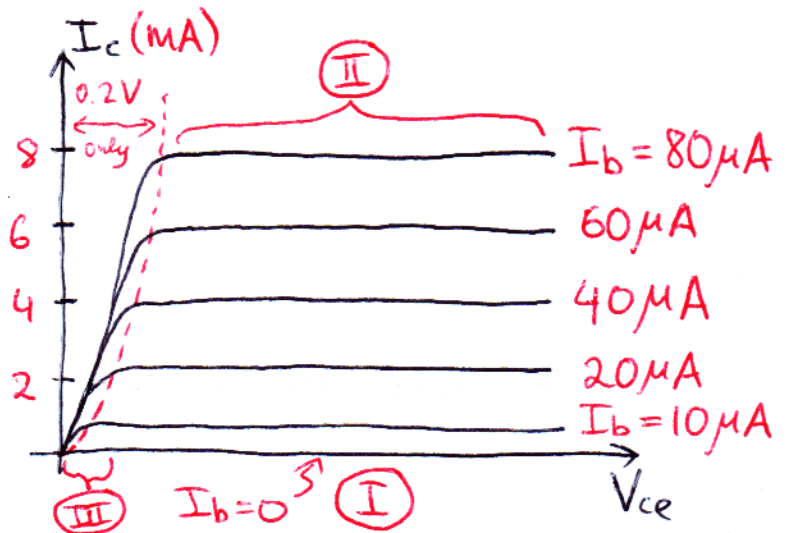

I cutoff (OFF) $I_b \sim 0$, $V_{be} < 0.6V$ (reverse), $I_c \sim 0$ ②
 \sim open circuit between C & e

II active
normal op. mode $I_b > 0$, $V_{be} \gtrsim 0.6V$ (forward)
 $V_{bc} \ll 0.4V$ (reverse)
 $I_c = \beta I_b$ ($\beta \gg 1$), I_c indep of V_{ce}
current controlled current source

III saturation (ON) $I_b > 0$, $V_{be} \gtrsim 0.6V$, $V_{bc} \gtrsim 0.4V$ (forward)
 $V_{ce-sat} \sim 0.1-0.2V$ (small) \uparrow check spec. sheets
 \sim short between C & e
 I_c is as large as external circuit allows

Important notes:

β - unreliable, varies with T, from transistor to transistor
parameter $\beta_{dc} = \frac{I_c}{I_b}$ $\beta_{ac} = \frac{\Delta I_c}{\Delta I_b}$

e.g. $\beta_{ac} \uparrow$ as $I_b, I_c \uparrow$ @ fixed V_{ce}


I_b 0.5-5 μA $\beta_{ac} \rightarrow 2\beta_{ac}$ } see
5-50 μA $\beta_{ac} \rightarrow 1.1\beta_{ac}$ } spec. sheets

β is guaranteed to be $\boxed{\beta \gg 1}$

Sometimes denoted by $\beta = h_{fe}$ \leftarrow other common notation
 β forward emitter


Transistor circuits

(3)

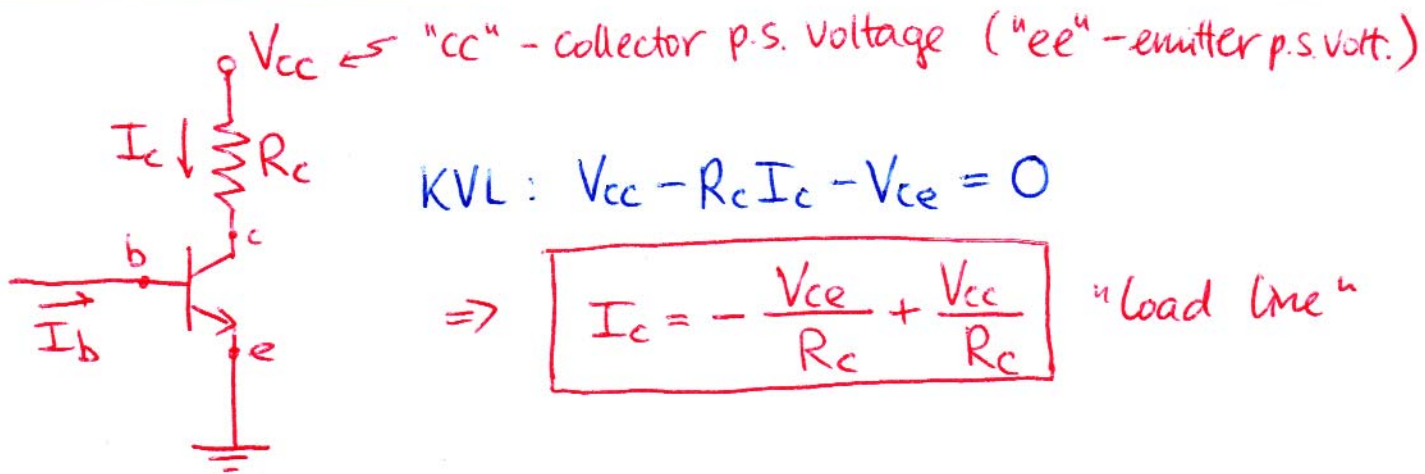

KVL: $V_{cc} - R_c I_c - V_{ce} = 0$

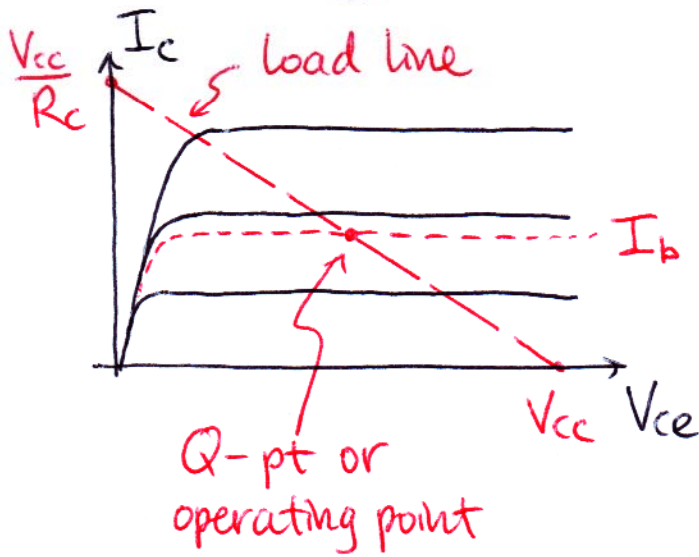⇒ $I_c = -\frac{V_{ce}}{R_c} + \frac{V_{cc}}{R_c}$ "load line"



- op. point (Q) constrained to lie on load line
- Q pt for V_{cc}, R_c fixed is determined by I_b

Transistor switch (a.k.a. saturating inverter)



- i) $V_{in} < 0V$, $I_b \approx 0$, $I_c \approx 0$ $V_{out} = V_{cc}$ (HI)
switch open

2) $V_m \gg 0.6V$ ($V_{be} \sim 0.6V$), $\Rightarrow I_b$ is large



(4)

V_{ce} ? see load line & I_c vs. V_{ce} plot \Rightarrow saturation

$V_{ce} \approx V_{ce-sat}$ (0.2V), $V_{out} = 0.2V$ (LO)
switch closed

Q: $I_c = \beta \cdot I_b$ when active. What if $I_c > \frac{V_{cc}}{R_c}$ (or $I_b > \frac{V_{cc}}{R_c \beta}$?)

A: transistor saturates

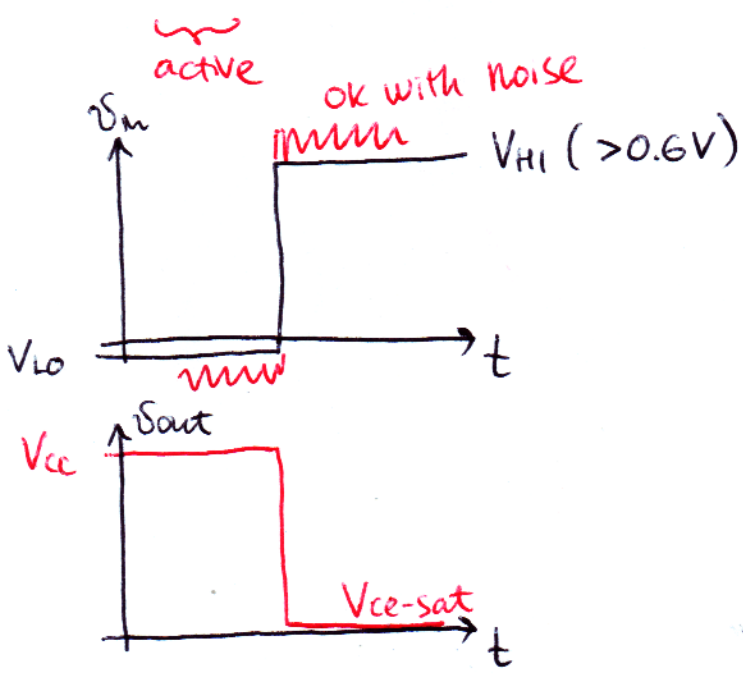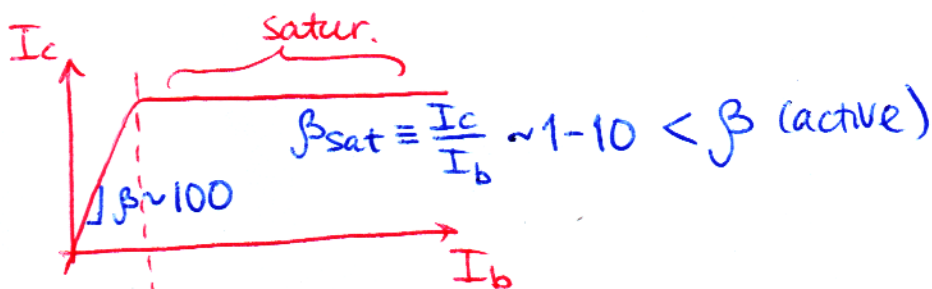

Important:

care must be given in choosing R_b
 $\beta_{min} < \beta < \beta_{max}$ (β value uncertain)

To ensure saturation for $V_m = V_{HI}$

choose

$$(I_b)_{sat} \geq \frac{(I_c)_{sat}}{\beta_{min}} = \frac{V_{cc}}{R_c} \frac{1}{\beta_{min}} \Rightarrow$$

$$I_b \cdot R_b = V_m - 0.6V$$

choose $R_b \leq \frac{V_{HI} - 0.6V}{(I_b)_{sat}}$