

Lecture 18


Transistor analysis (recap)

Two parts

① Large signal (Q-pt)

⇒ non-linear element transistor

- approx. of the actual transfer characteristics
- i)  $V_{be} < 0.6V$ ,  $I_b \sim 0$ ,  $I_c \sim 0$ ,  $I_e \sim 0 \rightarrow$  cutoff
  - ii)  $V_{be} \sim 0.6V$ ,  $V_{cb} > 0$ ,  $I_b \sim$  small  
 $I_c = \beta I_b \rightarrow$  active  
 $I_e \sim I_c$
  - iii)  $V_{be} \sim 0.6V$ ,  $V_{cb} \sim -0.4V \rightarrow$  saturation  
 $\beta_{sat} = \frac{I_c}{I_b} < \beta$ ;  $V_{ce} = V_{ce-sat} \sim 0.2V$

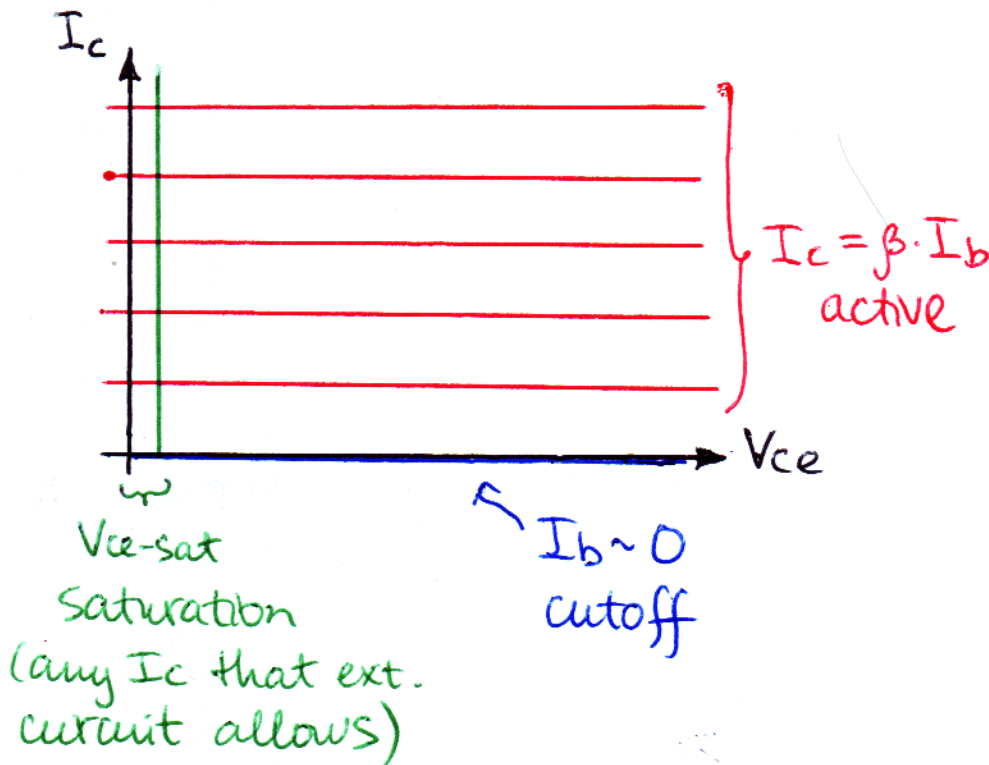


## ② Small-signal analysis

②

- makes sense if transistor is in active
- replace DC values  $\rightarrow$  0's;  $i_c = \beta \cdot i_b$ ,  $r_e = \frac{V_T^*}{(I_c)_Q}$
- linear behaviour

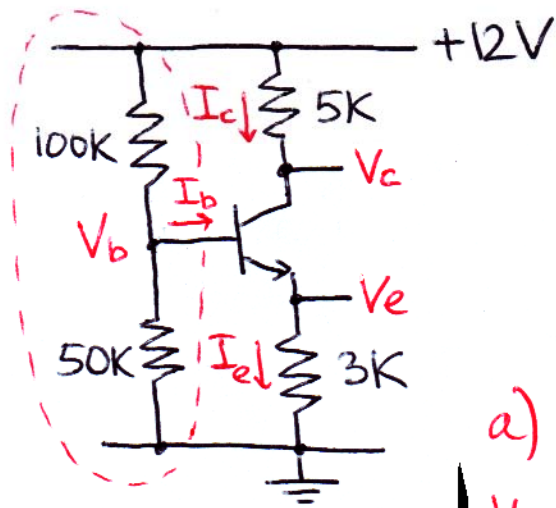Example: large signal analysis (Q-pt determination)



Find  $I_b, I_c, I_e$   
 $V_b, V_c, V_e$

Assume  $\beta = 100$ ,  $V_{be} \sim 0.6V$   
 $V_{ce-sat} \sim 0.2V$

Method 1)

a)  $\text{Ther. equivalent}$

$$V_{Th} = +12V \frac{50}{100+50} = +4V$$

$$R_{Th} = 100K \parallel 50K = 33.3K$$

b) assume Q = active (if not true, change your mind)

$$I_b = \frac{V_{Th} - V_b}{R_{Th}}, \quad I_e = I_b(\beta + 1) = \frac{V_e}{R_e} = \frac{V_b - 0.6V}{R_e}; \quad \text{Solve for } V_b, I_b$$

$$\Rightarrow V_b = 3.66V, \quad I_b = 0.010mA$$

$$V_e = 3.06V, \quad I_e = 1.031mA, \quad I_c = 1.021mA$$

Method 2) (method 1 is "too exact":  $\beta$  is known @ 10-20% level at best)

$$I_b \sim \text{small}, \Rightarrow V_b \sim 4V, \quad V_e \sim 3.4V, \quad I_e \sim 1.1mA \approx I_c$$

$$I_b = \frac{I_c}{\beta} \sim 0.011mA$$

$$V_{b, \text{new}} = V_{Th} - I_b R_{Th} \sim 3.6V \text{ (off by } 0.4V) \Rightarrow V_{e, \text{new}} = 3V$$

overall error due to  $I_b \rightarrow 0$  is 10% (good enough)