

P3360/AEP 3630

①

Lecture 19

↳ refer to the printout on Transistor Amp. Config.

Darlington Pair


Note:

-

-

-

# Power in transistors

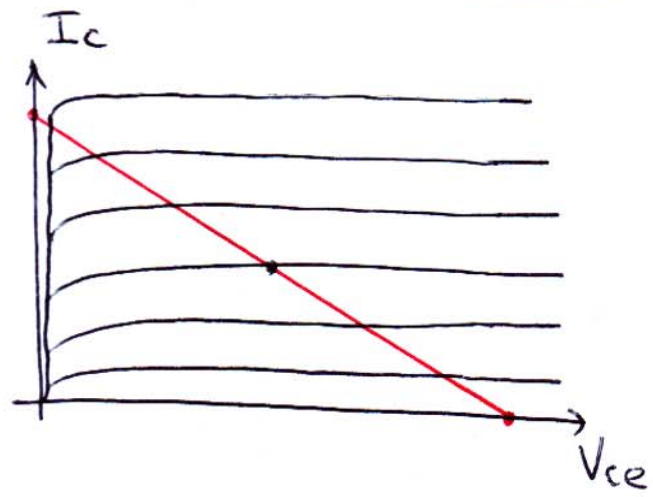

## class A amplifiers

- 
- 

pros :

cons :

## class B

- 

pros :

cons :

## class C

-