

P3360/AEP 3630

①

Lecture 19

↳ refer to the printout on Transistor Amp. Config.

Darlington Pair


Note:

-

-

-

Power in transistors

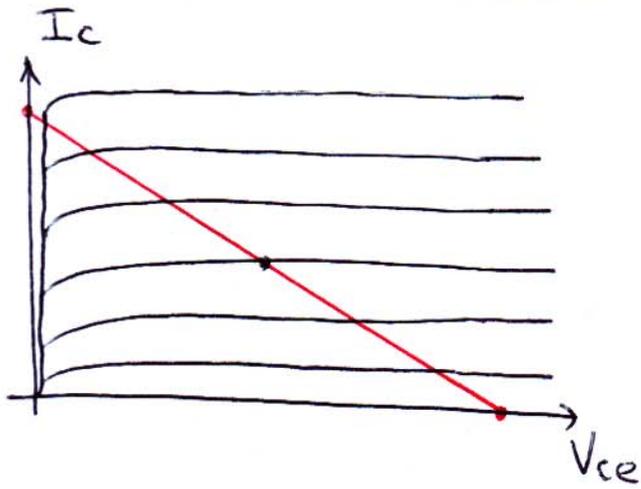

class A amplifiers

-

-

pros :

cons :

class B

-


pros :

cons :

class C

-


Notes on push-pull complementary stage

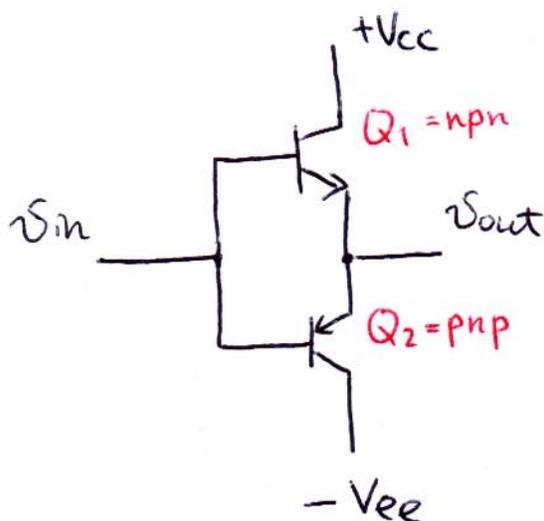

- "complementary" = both npn & pnp used
- "push-pull" only one transistor is ON (active), the other is OFF
- this is class B amplifier

- Note: both transistors cannot have forward biased be-junction simultaneously: $V_{be1} = V_{be2} = v_{in} - v_{out}$ b/c they are complementary

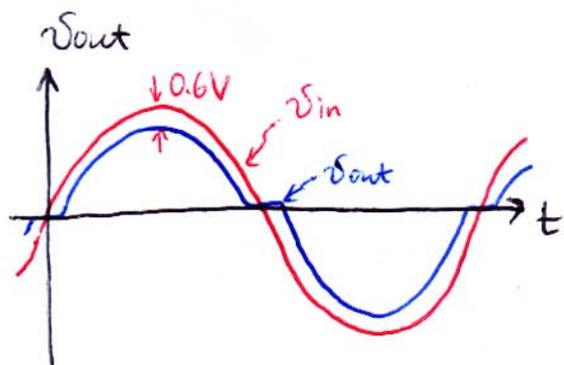- $G \sim 1$ for volt. , can have $G \gg 1$ for current




← Lab Manual, Fig 6.36

Note: there will be no cross-over distortions if no load is attached.


Q: why? A: no current can flow thru both $Q_{1,2}$, $\Rightarrow I_e \sim 0, V_{be} \sim 0$

With load:

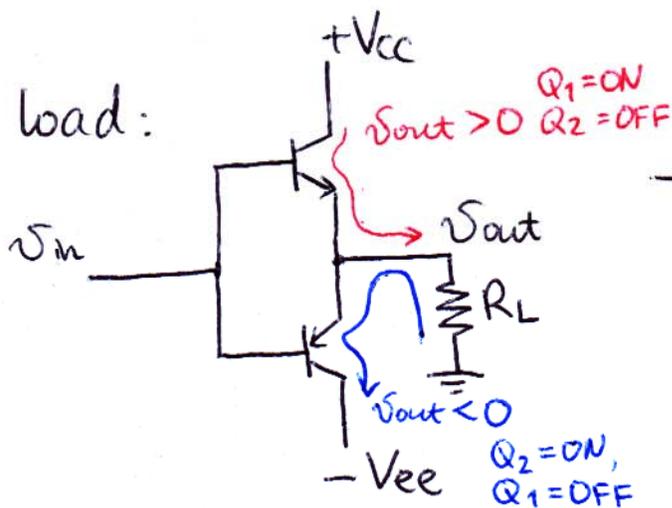

- the current flows in the direction of emitter arrows for half the cycle, the other transistor is OFF

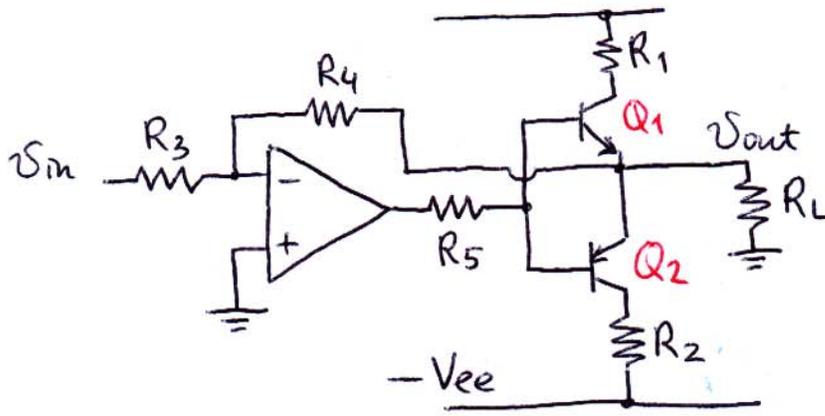Push-pull amp with negative feedback to fix cross-over dist.




- basic idea : eliminate 0.6V diode drop using negative feedback


← Lab Manual, Fig 6.37
Exp. 6.10

Steps to understanding this circuit:

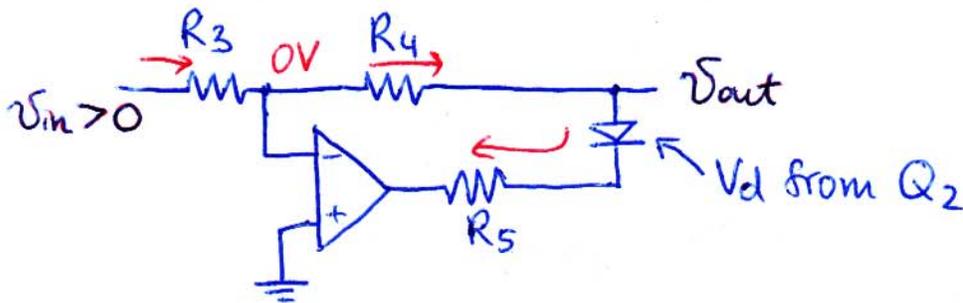- 1) negative feedback keeps $V_- = V_+$
- 2) when $V_m > 0$, the current flows to the right across R_3, R_4 , and Q_2 is ON



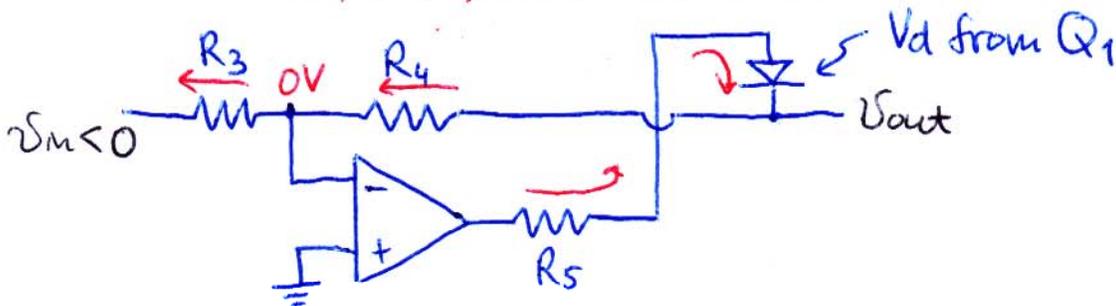- 3) when $V_m < 0$, the current flows to the left thru R_3, R_4 , and Q_1 is ON



In both cases
$$V_{out} = -R_4 \cdot I = -R_4 \frac{V_m}{R_3}$$

i.e. V_d does not come into the expression