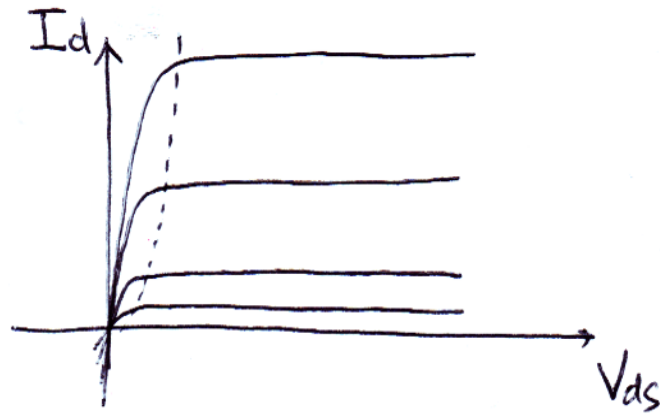


Lecture 21

MOSFET modes




mathematical model


If $V_{gs} < V_T$,

Else if $V_{ds} < V_{gs} - V_T$,


else,

Ohmic region

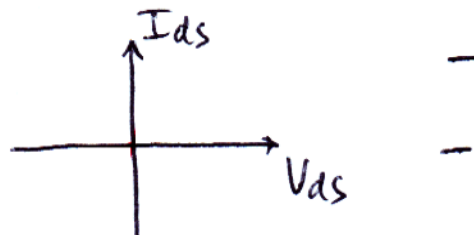

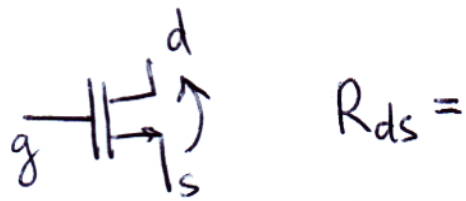

saturation (= active) region

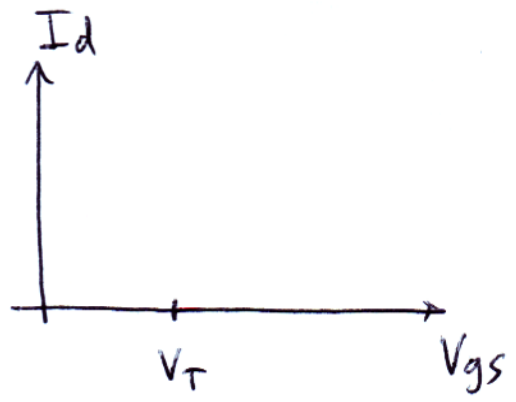

$$I_d = K(V_{gs} - V_T)^2$$

MOSFET circuit analysis

- ① large signal
- ② small-signal analysis

