

P3360/AEP 3630

①

Lecture 24

Boolean operations & gates

All digital operations can be reduced to

Gates =

-

-

-

NOT

AND


(2)

Multiple inputs AND

OR

Multiple inputs OR

Application of time dependent signal

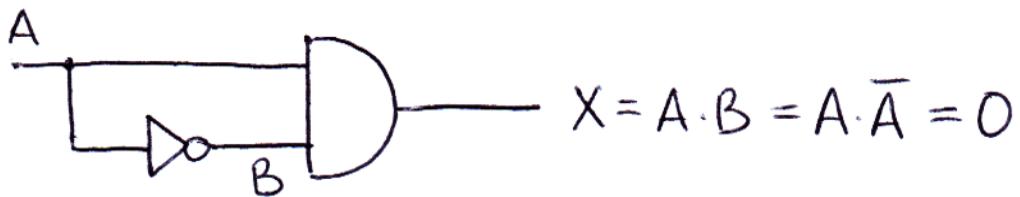

- any complicated fcn

-

-

Universal gates

-

-

-

NAND

NOR

(4)

De Morgan Theorem

Alternatively

Rules of Boolean algebra