 
 


Lecture 27

Combinational Logic

— outputs depend only on present values of inputs

Sequential Circuit (simple example)

- outputs depend on both present and states of memory (past) elements
- clock determines when info stored in memory can change

RS latch

recall NOR gate





if $A = 0$, $X = \overline{0 + B} = \overline{B}$,

\Rightarrow NOR becomes



②

  

S	R	Q	\bar{Q}
0	0	1	0
0	0	0	1
0	1	0	1
1	0	0	1
1	0	1	0
1	1	0	0
0	0	?	?

two stable states


reset

after $S=0, R=1$

set

after $S=1, R=0$

← contrary to the names ($Q=\bar{Q}$?)

 

summary


S	R	Q	\bar{Q}
0	0	no change	
0	1	0	1
1	0	1	0
1	1	not allowed	

— latch has asynchronous response, i.e. output changes whenever the input changes

— contrary to "flip-flop", which requires a clock.

Two stable states

(3)

 

- similar to ball analogy, need a strong enough force to send the latch from one stable state into another
- there exists a min pulse length needed for switching (typically ~ 10 's ns)

Flip-flop (i.e. clocked or synchronized clock)


problems with latches : asynchronous circuits
hard to combine/integrate

E.g. sequence of operations depends on exact values of prop. delays between gates

Synchronous circuits (= clocked) are usually preferred
Inputs/outputs change @ well-defined times

Improvements

1) clocked RS flip-flop

 

state can change only when $CLK=1$





2) triggering : level-sensitive or transition-sensitive (better)

$CLK (EN) = 1$
latch "transparent" when $CLK \nearrow$ or \searrow

Master-slave configuration

(4)

 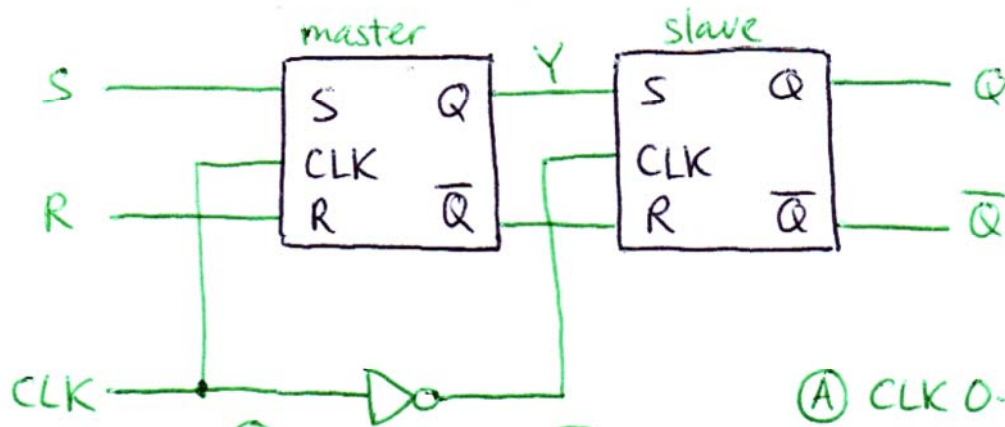


Ⓐ CLK 0 → 1 master enabled & slave disabled

Ⓑ CLK 1 → 0 master disabled & slave enabled


— Q ends up controlled by S, R when CLK ∇ only

— switch for multiple FF's can occur at the same time

Symbol

 


"+" edge ∇ triggered

 

"-" edge ∇ triggered

 3) direct inputs : used to set FF state asynchronously (= force a state)



PRE → 1 : Q → 1 } regardless of CLK, S, R
CLR → 1 : Q → 0 }