 


Lecture 25

XOR gate

A	B	X
0	0	
0	1	
1	0	
1	1	



Design procedure for combinational logic circuits

1) assign symbols

2) obtain boolean fcn

②

a)

b)

3) [optional]

4) draw the schematic

T	P	S	H
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

minterms -

maxterms -

output =

output =

Simplifying boolean expressions with Karnaugh maps (3)

Consider 2-input fcn

A	B	minterm
0	0	
0	1	
1	0	
1	1	

$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$
$A \cdot \bar{B}$	$A \cdot B$

$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$
$A \cdot \bar{B}$	$A \cdot B$

3-input fcn

4-input fcn


-

-

TP
 00 01 11 10
 S⁰
 1

Programmable logic devices

- used to implement

 

- can generate

-
 -

- some PLD types :