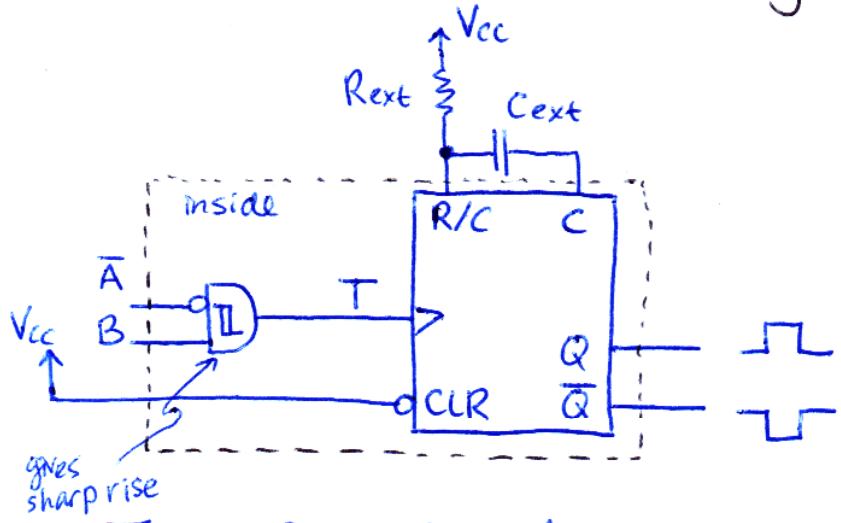


TTL (and variants) family of one-shots



74x221 dual non-retriggerable monostable multivibrator

$T_{HI} = R_{ext} \cdot C_{ext} \cdot \ln 2$; 50ns to 60s

| A | B | CLR | Q | Q-bar |
|----|----|-----|----|-------|
| LO | ↑ | HI | ⌊ | ⌋ |
| ⌋ | HI | HI | ⌊ | ⌋ |
| X | X | LO | LO | HI |

- see spec sheets for min/max R_ext / C_ext


555 can only do

- edge triggered one-shot (either ⌋ or ↑)
- trigger pulse longer than output OK (not so for 555)


74x123 retriggerable one-shot

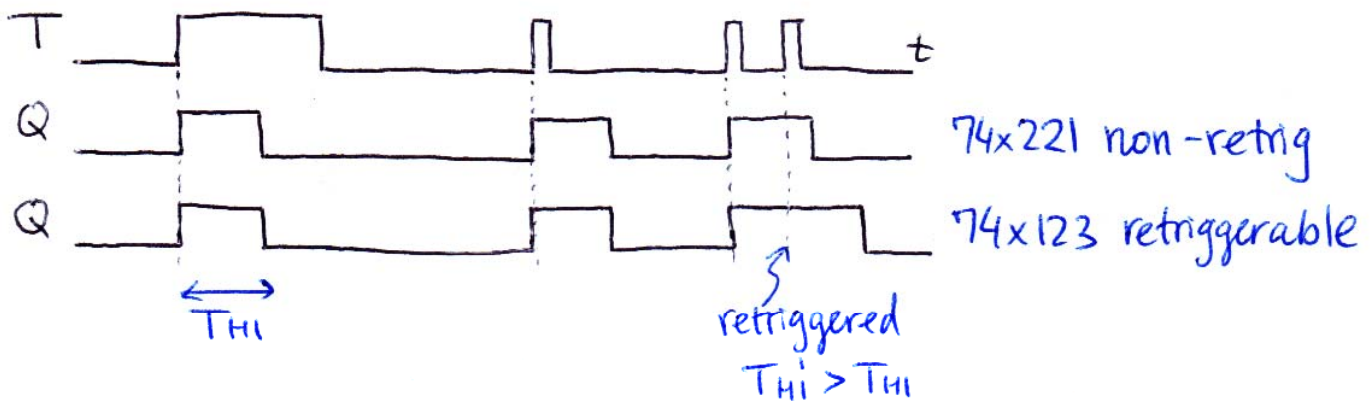(2)

other families
HC, HCT, LS
shottky
low power
TTL compat.
hybrid CMOS



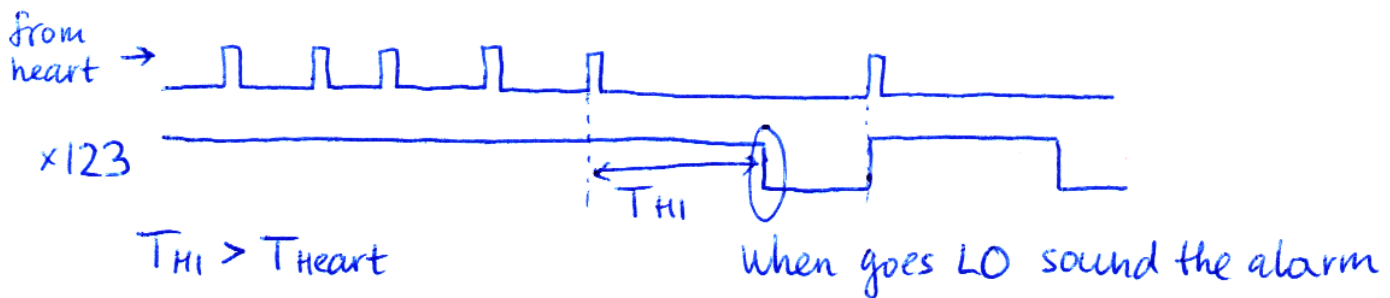Application: missing pulse monitor (a.k.a. heart monitor)




Use of one-shots

- convenient for small applications
- can be issues with noise immunity (part analog)
 - may misfire
 - long pulses \Rightarrow large caps \Rightarrow leakage current
 - timing accuracy is limited

3

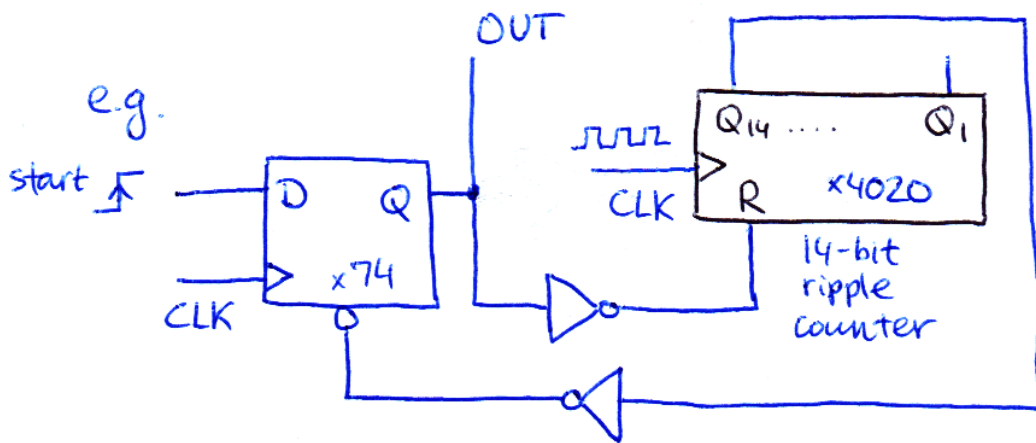Most functionality can be achieved with counters and precision clock




- OUT will stay HI $2^{14-1} = 8192$ clock ticks
- using combinational logic can program any delay up to 2^{14}
- all digital

Precision clocks

- 555 oscillator has limited accuracy ($\sim 1\%$)
ask (temp, pressure, humidity)
- often require much better accuracy
 - to remain precise within 30 min over a couple of years (to record a TV show) $\Rightarrow \sim 10^{-5}$ accuracy
 - key to a number of applications

Quartz Crystal oscillators


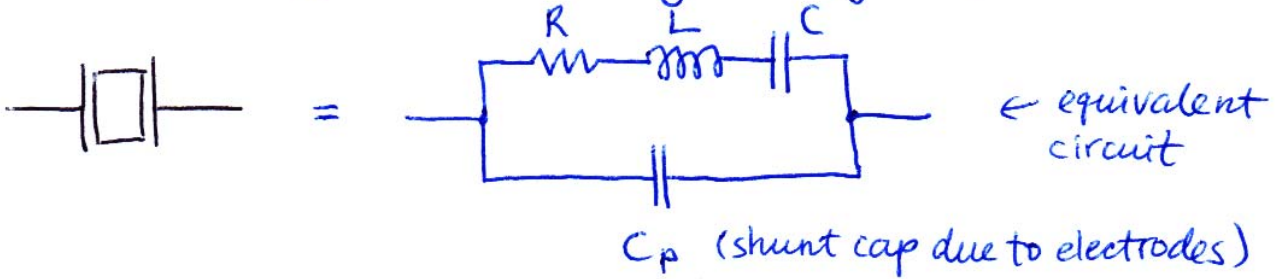
uses Piezo effect : stress \leftrightarrow electricity
to define reference frequency with great precision



- weak dep. of R, L, C on temperature, etc.

- recall : oscillations require loop gain ≥ 1 & loop phase 360° (or 0°) (incl. 180° from neg. FB)

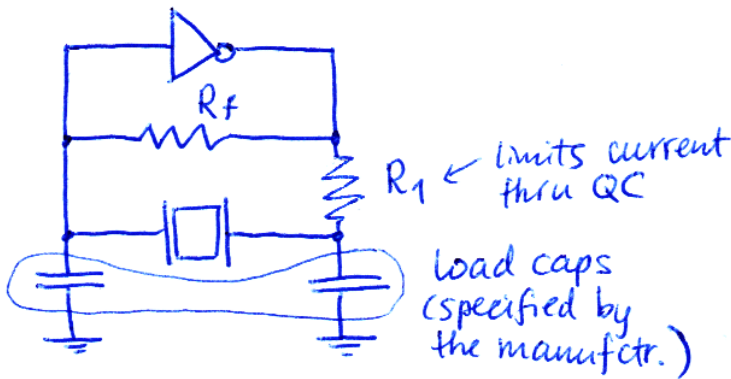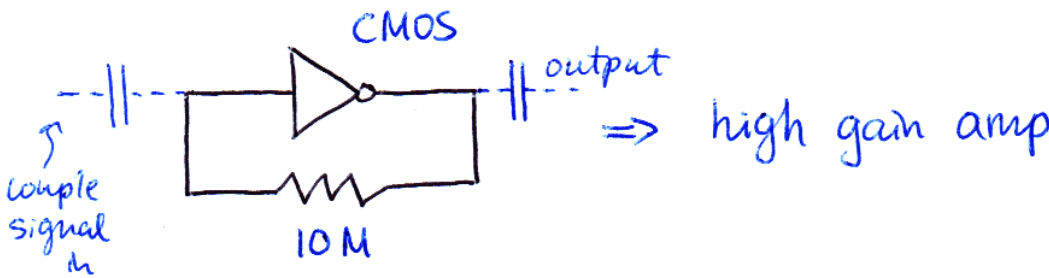- QCO meets the phase req. @ specific frequency



- available as a single chip

- few kHz to 100's of MHz

- accuracy 1 sec over 30 years

(still need temp. control, etc. to achieve the best results)