

## Lecture 36


A/D and D/A converters

-  
-

$\Rightarrow$

Digital representation of info

-  
-

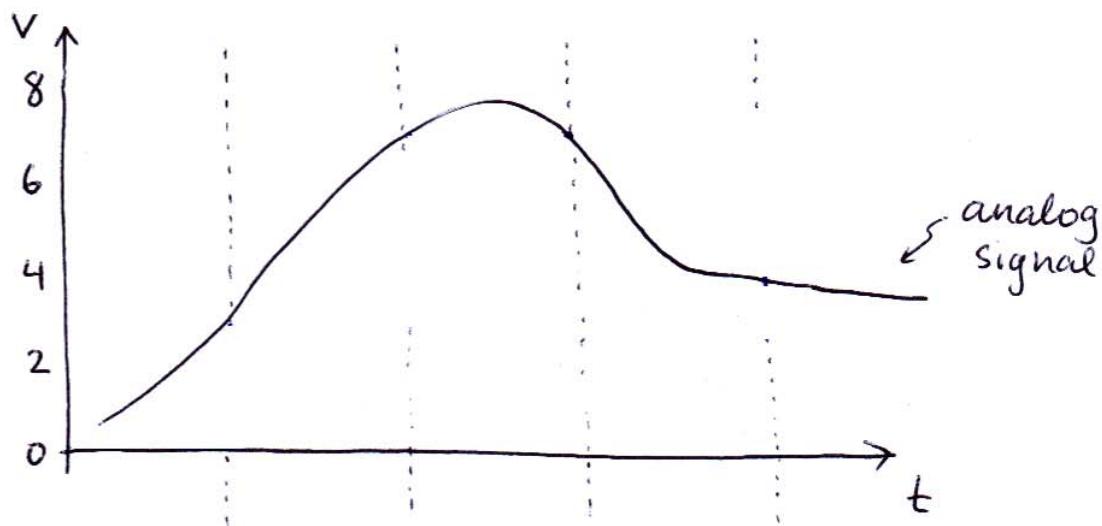

- both \_\_\_\_\_ and \_\_\_\_\_ affect fidelity of representation


i) # bits

(2)

2) sampling rate

### D/A conversion

recall summing circuit

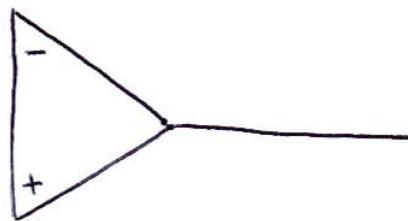

Assume

Problems


(3)

1)

2)

3)

R-2R ladder D/A converter

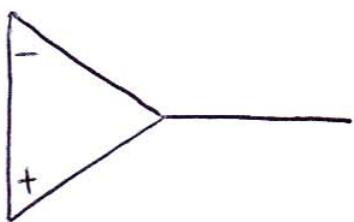

starting from LSB

(4)

- widely used