 


Lecture 38

 Σ - Δ modulator (ADC)

- Σ - Δ name comes from adding (Σ) v_{in} and subtracting 1-bit DAC output (Δ) v_{DAC}
- unlike other ADC types, Σ - Δ is closed loop config.
- negative feedback theory: $\langle v_{DAC} \rangle \rightarrow v_{in}$
- (parallel) binary output is obtained by averaging the serial bit stream (e.g. use counter to collect the total # of 1's over a fixed # of clock ticks)

Refer to the schematic (the printout)


- op-amp #1 : summing integrator (v_{in} subtracted, \Rightarrow inverted bit stream)
- op-amp #2 : 1-bit ADC
- op-amp #3 : shift 0/5V to -V/+V signal

Ex. integrator output is high, $v_{DAC} = +V$, pulls the integ. low until $\langle v_{DAC} \rangle \rightarrow -v_{in}$. see trace examples / LTspice

Nyquist sampling criterion & aliasing

 (2)

Q: basic question - what must the sampling rate be to accurately represent signal at frequency f ?



• $f_s = 2f$ ($= \frac{1}{t_s}$)

□ $f_s = \frac{4}{3}f$

- if $f_s > 2f$, no aliasing occurs


⇒ Nyquist theorem: choose $f_s > 2f_{\max}$

highest freq. in the signal

- if $f < f_s < 2f$, aliasing

$$f_a = f_s - f$$

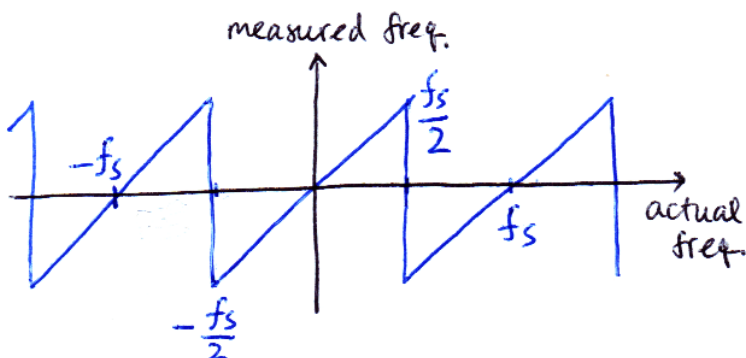- if $f_s < f$, aliasing $f_a = f_s - f \pmod{f_s}$



Q: how to avoid aliasing?

A: use LP filter $< \frac{f_s}{2}$

Effect of conversion time (t_c) on resolution

$$v_m = v_o \sin(2\pi f t) \leftarrow \text{digitize with } n\text{-bit resolution}$$

What is the largest f for v_m to change less than 1LSB in time t_c ?

$$V_{p-p} = 2v_o, \text{ resolution } \frac{V_{p-p}}{2^n - 1} = \Delta v_r$$

$$\Delta v_r = \left. \frac{dv_m(t)}{dt} \right|_{\max} \cdot t_c = 2\pi f v_o t_c, \Rightarrow$$

$$\boxed{f \leq \frac{1}{\pi} \frac{1}{2^n - 1} \frac{1}{t_c}} \quad \text{otherwise, the resolution is lost}$$

E.g. 8-bit ADC with $t_c = 10\mu s$ (100kHz)

\Rightarrow will digitize to 8-bit accuracy only if $f \leq 125 \text{ Hz}$ (not 100kHz!)


Effective resolution can be substantially worse than bit resolution for fast signals

- there may be no sense in choosing higher-bit ADC for a given f/t_c combination

Q: newest scopes can digitize at 20GHz (~50ps). How?
No ADC is that fast!

Sample & hold circuit (see the printout)

 - use "fast memory" to record the trace, digitize later



S is hi-speed FET switch
 v_{out} holds v_c after
 S is opened

General A/D converter layout (see the printout)

Digital scopes

Sampling

- 100GHz BW doable
- very high BW is achieved via reconst. of repetitive signal on multiple passes with variable delay

Real-time

- max BW 20GHz (typically < 1GHz)
- acquire the whole trace in a single shot using sample & hold; then A/D convert