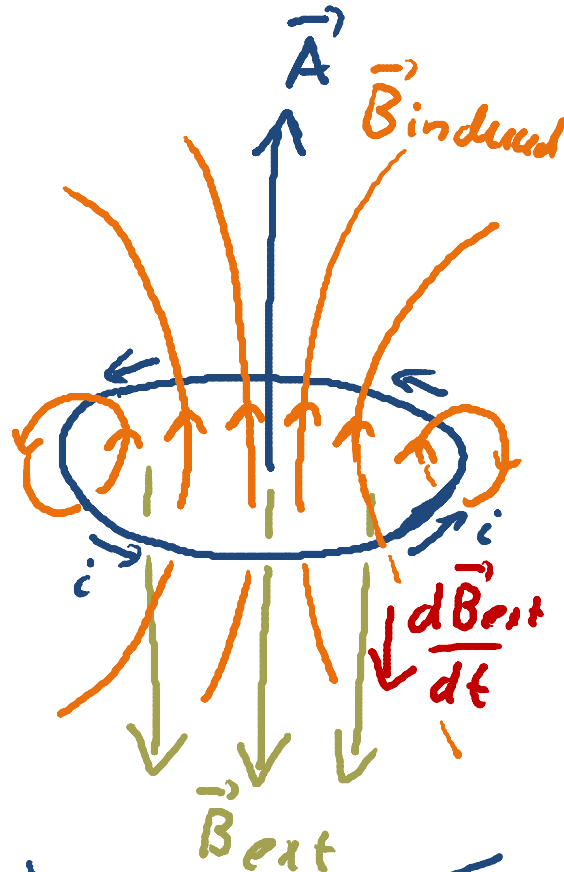


Magnetic Induction:



- Emf induced by changing flux through a conducting loop:

Faraday's Law $\mathcal{E} = - \frac{d\Phi_{B, \text{through loop}}}{dt}$

- resulting induced current:

$i_{\text{ind}} = \frac{\mathcal{E}}{R}$ ← Resistance of the loop

- Lenz's Law: An induced current has a direction such that the magnetic field due to the induced current opposes the change in the magnetic flux that induces the current.


$\Phi_B = \vec{B} \cdot \vec{A} < 0$ here

$d\Phi_B/dt < 0$ here $\Rightarrow \mathcal{E} > 0$

\Rightarrow current flows in "direction"

Today:

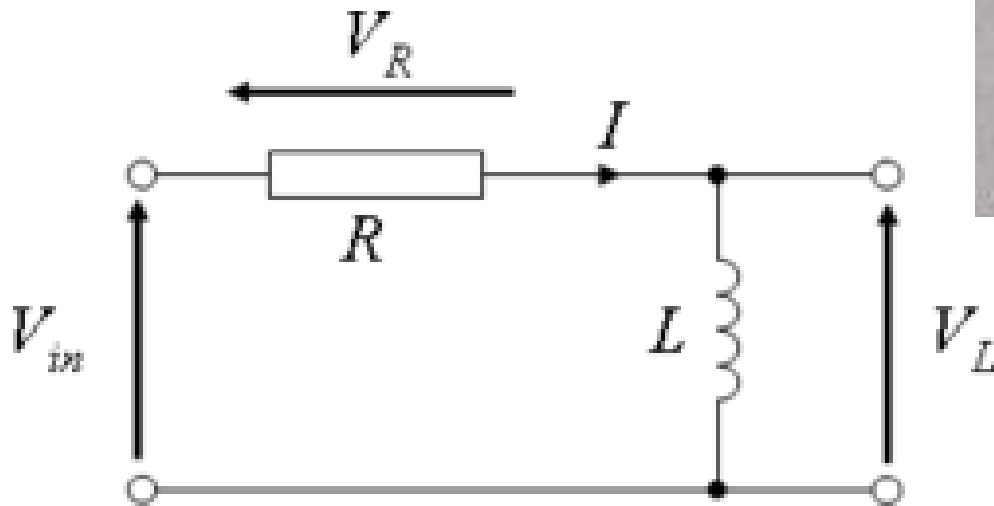
- Inductors and their inductance
- RL circuits
- Energy density of a magnetic field



Inductors and Inductance L:

→ Recall: Capacitors and Capacitance

- Capacitor: produces electric field between two plates

- Symbol: 

- Described by capacitance: $C = \frac{Q}{\Delta V_c}$ } depends on geometry of capacitor

- Energy of electric field in capacitor: $U = \frac{1}{2} C \Delta V_c^2$


→ Now:

- Inductor: produces a magnetic field around current carrying wire

- Symbol: 

- Described by inductance L

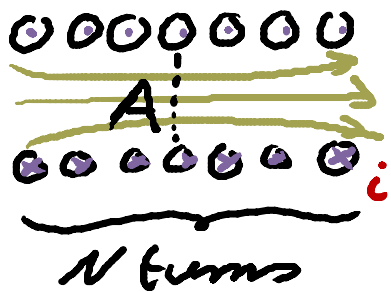→ Consider a solenoid with N windings / turns:



- magnetic flux through central region of area A : Φ_B

- some flux goes through each winding of solenoid \Rightarrow are "linked" by shared flux

- define magnetic flux linkage = $N\Phi_B$

• Define Inductance L of solenoid / inductor:

$$L \equiv \frac{N\Phi_B}{i}$$



number of turns of wire

current going through wire

Units:

$$\underline{\underline{[L]}} = \frac{[\Phi_B]}{[i]} = \frac{\text{Tm}^2}{\text{A}} = \text{1 henry} = \underline{\underline{1 \text{ H}}}$$

Self-induction in an Inductor:

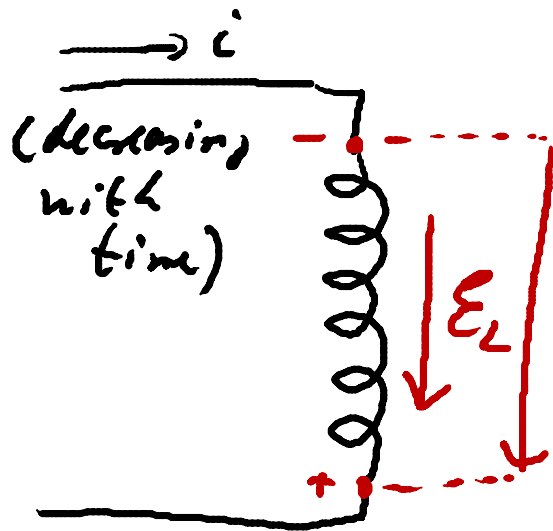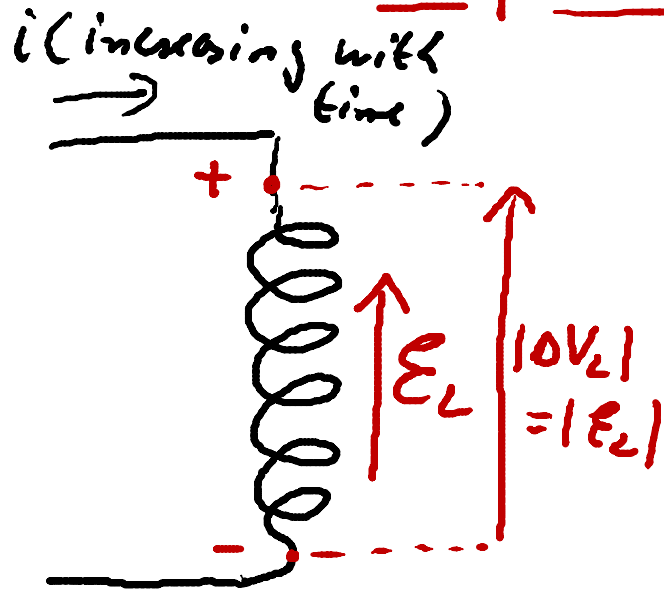

suppose that we let current i in the solenoid change with time

⇓
magnetic flux Φ_B changes with time

⇓
according to Faraday's law: an emf will be "self-induced" in the solenoid, that opposes the change in (current) flux
(note: only one solenoid involved here!)

for ideal inductor without resistance R in wire

=> from Faraday's Law:

$$\underline{\mathcal{E}_L} = -N \frac{d\Phi_B}{dt} \quad \text{for solenoid with } N \text{ turns}$$

$$= - \frac{d(N\Phi_B)}{dt} = - \frac{d(Li)}{dt} \quad \text{since } L = \frac{N\Phi_B}{i}$$


$$= - \underline{L \frac{di}{dt}}$$

=> if current is changing in an inductor ($\frac{di}{dt} \neq 0$)
then there is a self-induced emf in the inductor:


$$\mathcal{E}_{\text{self-induced}} = -L \frac{di}{dt}$$

rate of change of current i

RL circuit: Rise of current

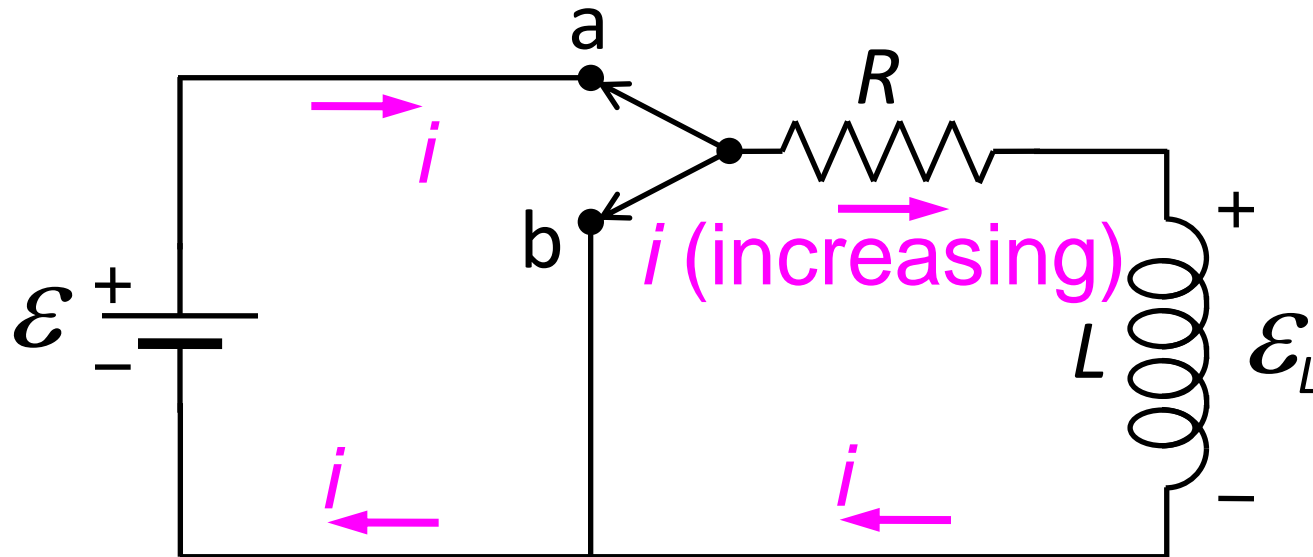

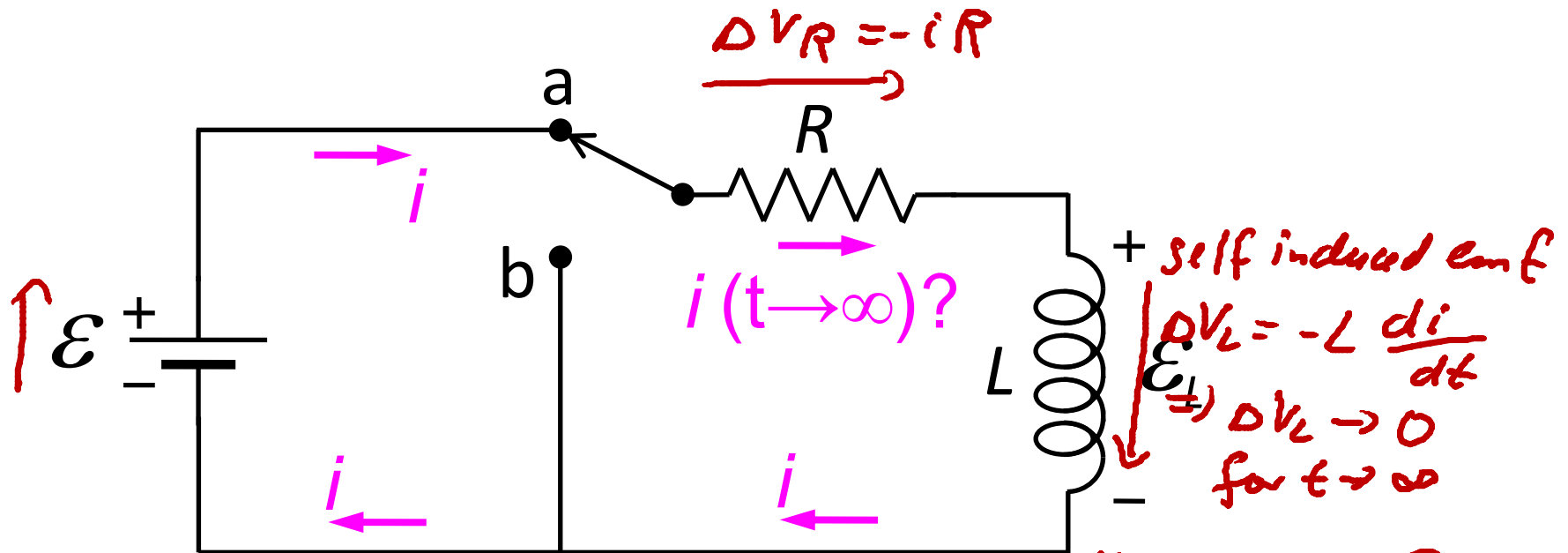- At time $t = 0$ move the switch to position a.
 - Current i begins to flow but the self-induced emf \mathcal{E}_L in the inductor L opposes the rise in current.
- > **Current starts out at 0 at $t=0$ and then increases until it approaches a steady state value asymptotically.**



loop rule: $\mathcal{E} + \Delta V_R + \Delta V_L = 0 = \mathcal{E} - iR - L \frac{di}{dt} \Rightarrow i = \frac{\mathcal{E}}{R}$


At time $t = 0$ move the switch to position a. for $t \rightarrow \infty$

After a very long time what will be **the magnitude of the steady state current** in the circuit?

$i = \text{const} \Rightarrow \frac{di}{dt} = 0 \rightarrow 0$

- A. 0
- B. $|\mathcal{E}_L|/R$
- C. \mathcal{E}/R**
- D. $(\mathcal{E} - |\mathcal{E}_L|)/R$**
- E. Both answers C & D above.**

RL circuit: Rise of current

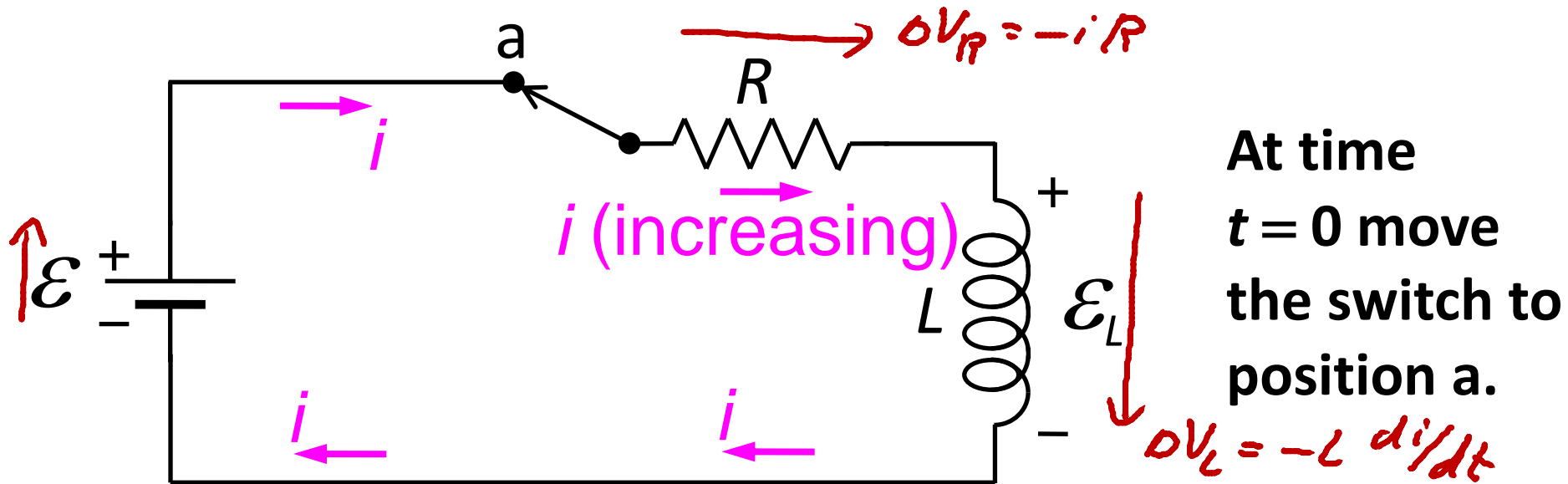

Use loop rule: $\mathcal{E} + \Delta V_R + \Delta V_L = 0$

$$\Rightarrow \mathcal{E} - iR - L \frac{di}{dt} = 0 \quad \left. \begin{array}{l} \text{differential equation} \\ \text{for current rise} \end{array} \right\}$$

$$\text{at } t=0 : i(t=0) = 0 \quad \left. \begin{array}{l} \text{initial condition} \end{array} \right\}$$

$$\Rightarrow \text{Solution: } i(t) = \frac{\mathcal{E}}{R} \left[1 - e^{-\mathcal{E}R/L} \right]$$

$$\text{check: } i(t=0) = 0 \quad \checkmark \quad \frac{di}{dt} = + \frac{\mathcal{E}}{L} e^{-\mathcal{E}R/L}$$

RL circuit: Rise of current

Current in inductor

$$i(t) = \frac{\mathcal{E}}{R} [1 - e^{-t/\tau}]$$

with time constant
of current increase

$$\tau = L/R$$





Change in electric potential across the inductor

$$|dV_L| = L \frac{di}{dt} = \mathcal{E} e^{-t/\tau}$$


Note: • at $t=0$, $i=0$ and $|dV_L| = \mathcal{E}$

• at $t \rightarrow \infty$, $i = \frac{\mathcal{E}}{R}$ and $|dV_L| = 0$

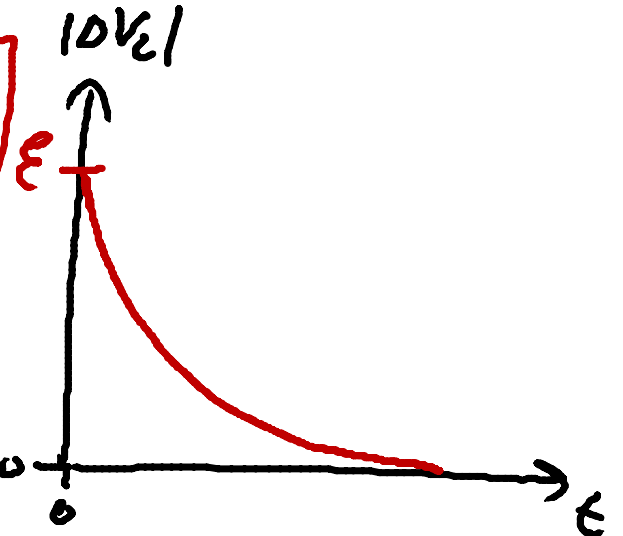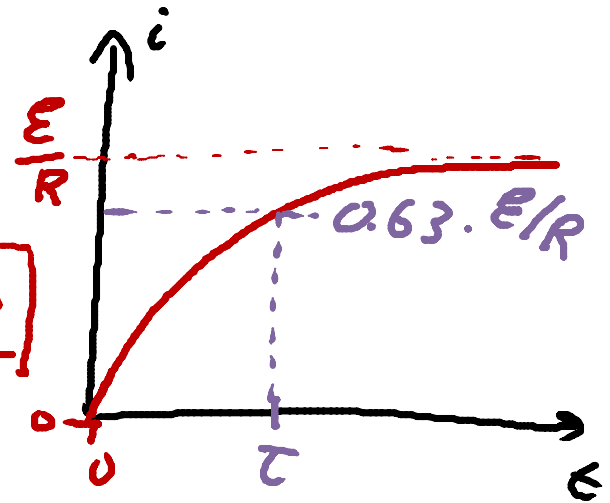i.e. inductor eventually behaves like an ordinary connecting wire




RL circuit: Decay of current

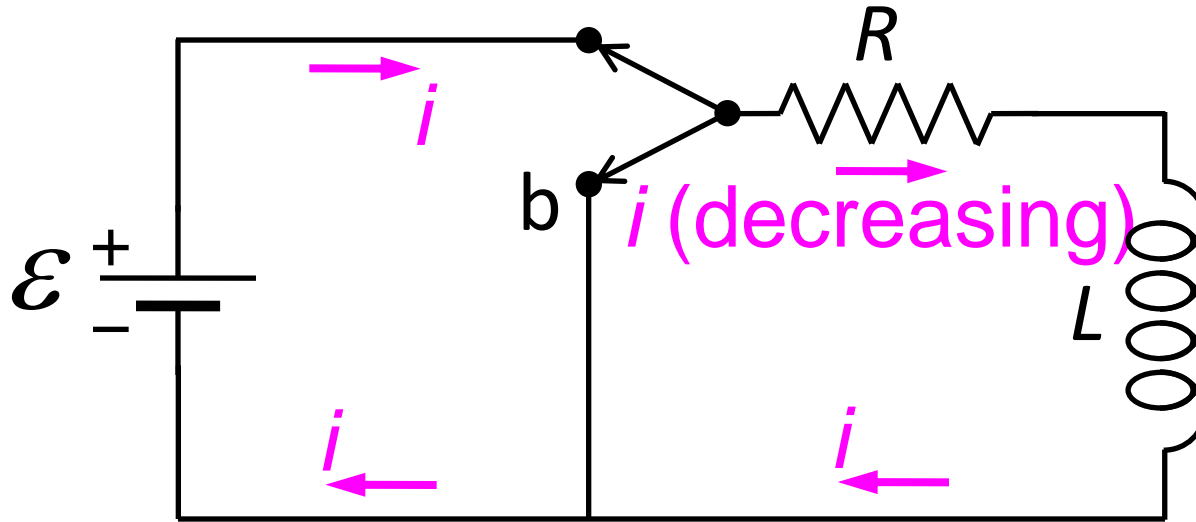

- The switch has been in position a for a very long time.
 - At time $t = 0$ move the switch to position b.
 - Current i begins to decrease, but the self-induced emf \mathcal{E}_L in the inductor L slows down the decrease in current.
- > **Current starts out at the equilibrium value, and then decays to zero over time.**

RL circuit: Decay of current

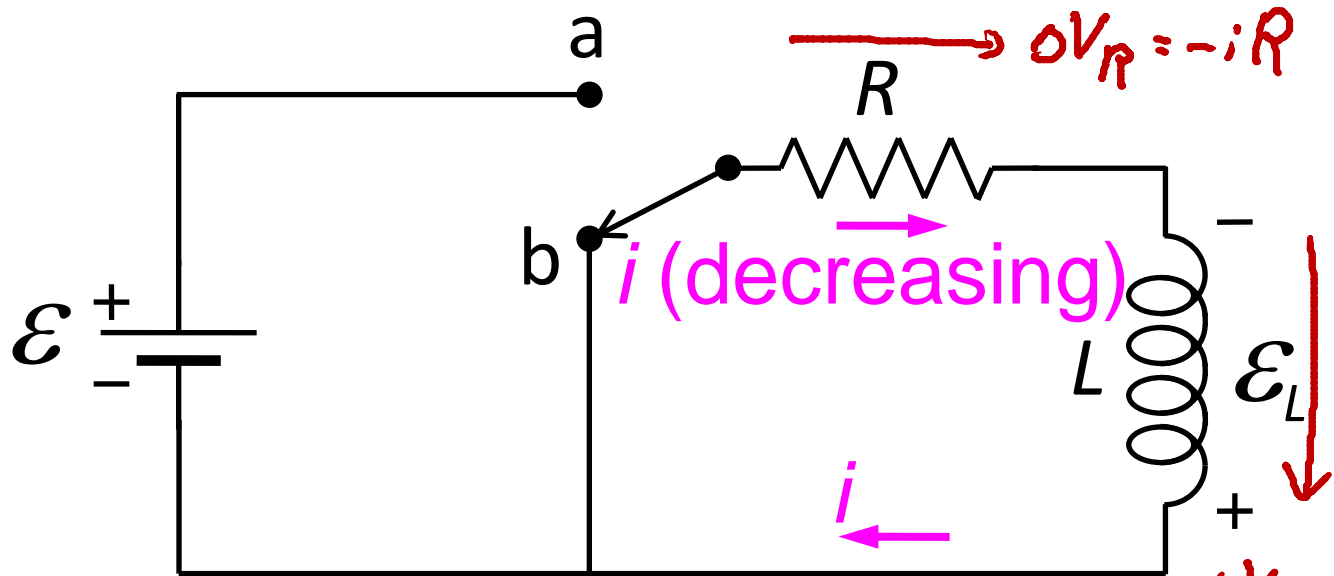

At time $t = 0$, switch to position b using a make-before-break switch.

use loop rule: $\Delta V_R + \Delta V_L = 0$

$\Rightarrow -iR - L \frac{di}{dt} = 0$ } differential equation for current decay

at $t=0$: $i(t=0) = i_0$ } initial current

\Rightarrow solution: $i(t) = i_0 e^{-tR/L}$

check: $i(t=0) = i_0$

$$\frac{di}{dt} = -\frac{i_0 R}{L} e^{-tR/L}$$

$\Delta V_L = -L \frac{di}{dt}$
 < 0 now!

RL circuit: Decay of current

current in
inductor :

$$i(t) = i_0 e^{-t/\tau}$$

with time constant $\tau = L/R$
for current decay

change in
electric potential
across the
inductor

$$|dV_L| = \left| L \frac{di}{dt} \right| \\ = i_0 R e^{-t/\tau}$$

Note:

if current has reached steady
state value $i = \mathcal{E}/R$ before
moving switch to position b:
 $i_0 = \mathcal{E}/R \Rightarrow |dV_L(t=0)| = \mathcal{E}$

